



Real-Valued Verilog Models for Analog Circuits

Prof. Chien-Nan Liu
Institute of Electronics
National Chiao-Tung Univ.



Tel: (03)5712121 ext:31211
E-mail: jimmyliu@nctu.edu.tw
<http://mseda.ee.nctu.edu.tw/jimmyliu>

Outline

- ◆ Introduction
- ◆ Real-Valued Behavioral Models in Verilog
- ◆ Portable Models for Verilog/Verilog-A
- ◆ Test Results
- ◆ Conclusions


Difficulty in Mixed-Signal Verification

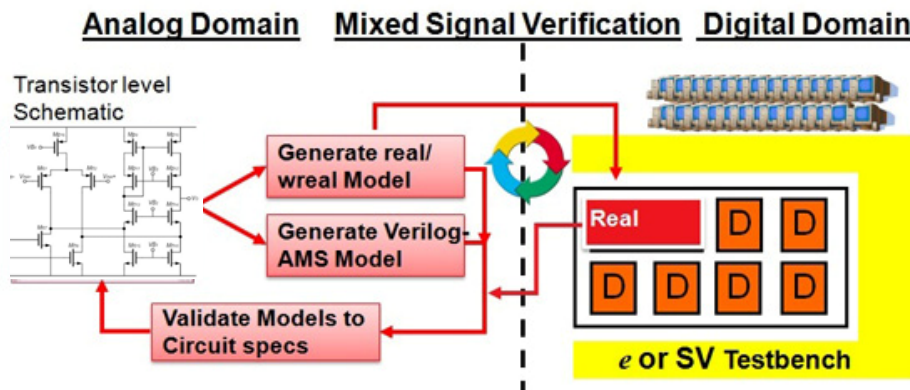 - ◆ Opposite circuit design/verification flow
 - Analog: Bottom-up; Digital: Top-down
- ◆ Use behavioral model to replace the analog part
 - Only way for system-level verification



Behavioral Model

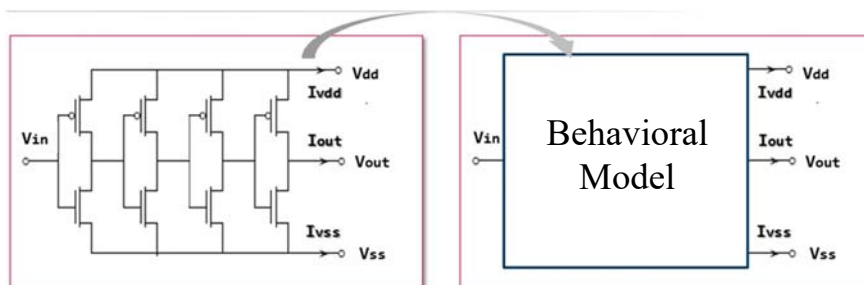
- ◆ A simplified circuit block that model of the same input-output functionality
 - Capture just the essential behaviors
- ◆ Adjustable equation-based verification
 - Composed of circuit equations
 - Modified by different size, process variation...
- ◆ Tradeoff between **accuracy** and **speed**



Modeling Strategy is Important

- ◆ Different abstraction will result in different runtime, even the same language (ex: Verilog-A) is used !!

Equivalent Circuit Model

 

```
I(N,vss) <+ -Gm*V(inp,inm);
I(N,vss) <+ (V(N,vss)-V(vdd,vss)/2)/Rres;
I(N,vss) <+ ddt(Ccap*V(N,vss));
I(N,vss) <+ `fclip(V(N,vdd),1,40m)
          - `fclip(V(vss,N),1,40m);
I(N,out) <+ V(N,out) / Rac;
```

Fully Behavioral Model

```
module opamp (vout, vin_p, vin_n );
  inout vin_p, vin_n;
  output vout;
  electrical vin_p, vin_n, vout;


  analog begin

    I(vin_p) <+ 0.0;
    I(vin_n) <+ 0.0;
    V(vout) <+ V(vin_p, vin_n) * Av;
  end
endmodule
```

Fast!


Why Using Verilog Model ?

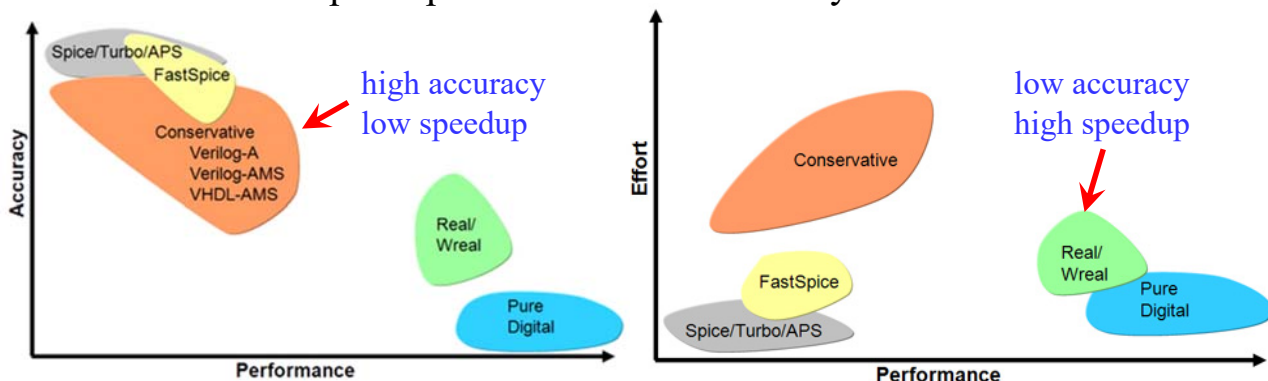- ◆ Verilog-A does not fit well in a pure digital event-driven validation framework
 - Although accuracy is good with Verilog-A models, the gained speedup is limited
- ◆ Real-valued Verilog model provides another solution
 - Further speedup with sacrificed accuracy




Adv. of Real-Valued Verilog Model

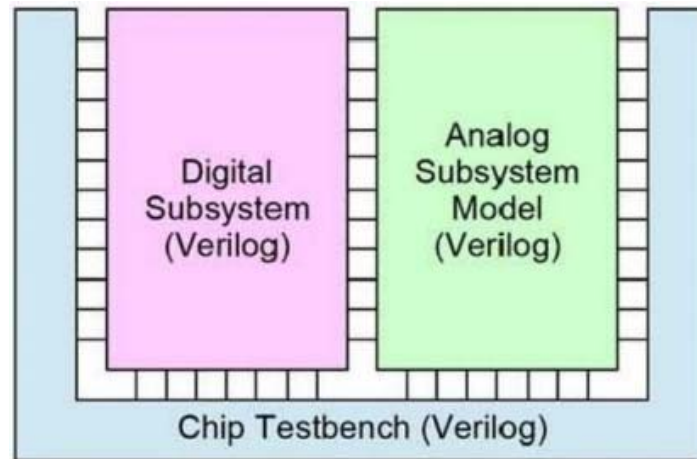- ◆ Provide pin-accurate behavioral model for system-level validation in the **same environment**
 - Assertion-based verification (ABV) and metric-driven verification can also be applied in mixed-signal simulation
- ◆ Portable between digital and analog design environments



Adv. of Real-Valued Verilog Model

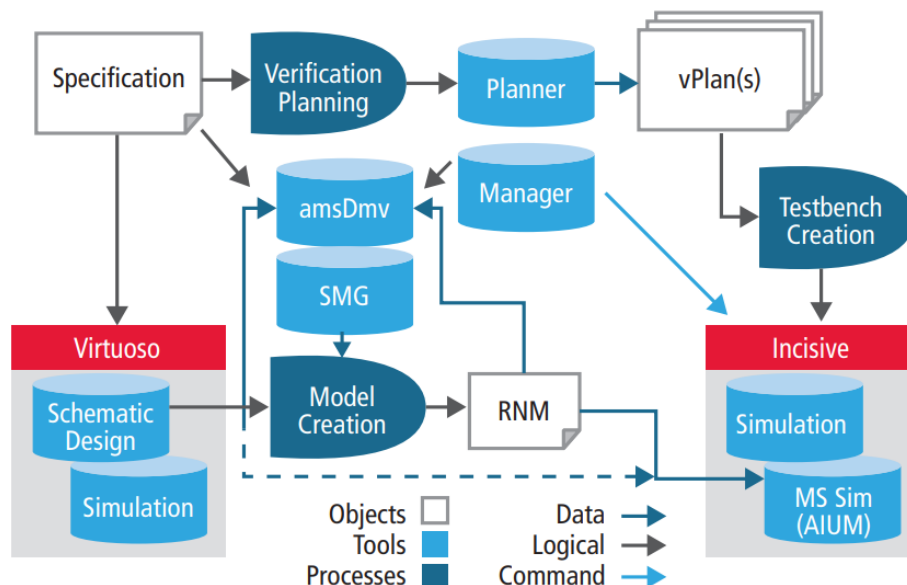
- ◆ Full-chip verification can be run with digital solvers
- ◆ Rapid simulation even for large SoCs
 - If accuracy loss is acceptable



Adv. of Real-Valued Verilog Model


- ◆ Still able to model parasitic coupling

 - Although several approximations are required with Verilog



- ◆ No need for iterative analog SPICE engine

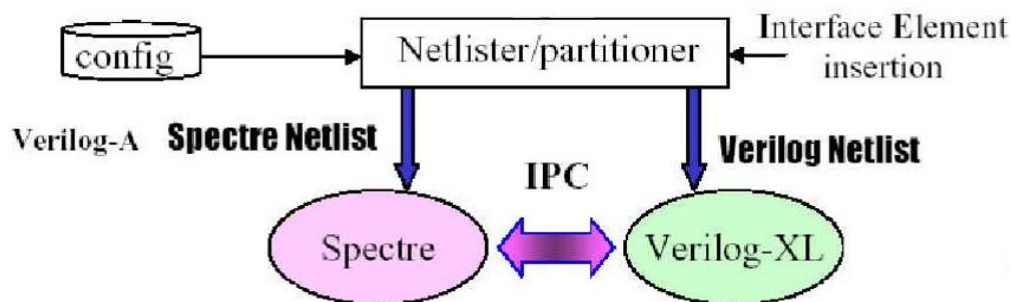- Eliminate the communication between different engines



Ref: CIC training manual

Difficulty to Model Analog Behaviors

- ◆ Operators are limited in digital languages


- Timing parameters: rise/fall time? slew rate?
- Math operators: differential? integral? Laplace transform??
- A per-timestep format is often required for approximation

- ◆ Interface between modules require special handling

- Only support digital ports --- wire/reg (0 & 1)
- PWL or RNM waveforms

$$\int_{x_a}^{x_b} f(x) dx$$

$$\frac{d}{dx} a^x$$

 


electrosfts.com

Outline

- ◆ Introduction
- ◆ Real-Valued Behavioral Models in Verilog
- ◆ Portable Models for Verilog/Verilog-A
- ◆ Test Results
- ◆ Conclusions

Represent Continuous-Time Signals

 - ◆ Two popular approaches to represent analog signals in a digital simulator
 - Piecewise-constant (PWC)
 - Piecewise-linear (PWL)



Ref: S. Liao and M. Horowitz, "A Verilog piecewise-linear analog behavior model for mixed-signal validation," IEEE TCAS-I, vol. 61, no. 8, pp. 2229–2235, Aug. 2014.

Model Comparison

◆ Real-valued models

➤ Difference equations


$$\Delta V_{out} = \Delta t \frac{I_r}{C}$$

$$I_r = (V_{in} - V_{out})/R$$

◆ Accurate for small steps

◆ Much faster simulations

◆ Ex: RC filter

 

◆ Verilog-A models (slow)

➤ Differential equations

$$dV_{out} = dt \frac{I_r}{C}$$

$$I_r = (V_{in} - V_{out})/R$$

➤ Simulator chooses Δt

```
input Vin;      // input voltage
real Ir;        // resistor current
real Vout;      // output voltage
real lsttim;    // last time model was evaluated

initial begin
    Vout = 0.0;
    lsttim = 0.0;
end

Ir = (Vin - Vout) / R;
Vout = Vout + Ir * ($abstime - lsttim) / C;
lsttim = $realtime;
```

Δt is user specified

Ref: Bill Ellersick, "Real Portable Models for System/Verilog/A/AMS", SNUG 2010

P.13

Another Way: Discrete Transfer Function

◆ In Laplace notation, the transfer of a RC low-pass filter is

$$H(S) = K / (\tau S + 1), K = \text{filter gain}, \tau = \text{time constant}$$


◆ Using Bilinear transform, its z-transform function is

$$H(z) = K * (n_0 + n_1 z^{-1}) / (d_0 + d_1 z^{-1}), \text{ where } n_0 = n_1 = 1$$

$$d_0 = 1 + 2\tau / T_s, d_1 = 1 - 2\tau / T_s \quad (T_s = \text{sampling rate})$$


◆ So, **$OUT_{new} = K * (IN_{new} * n_0 + IN_{old} * n_1 - OUT_{old} * d_1) / d_0$**
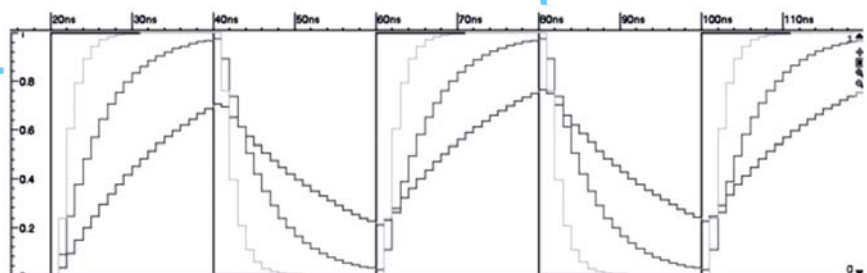
```
always #(Ts) begin // sample input every Ts
    OUTval = K * (IN + INold - OUTval * d1) / d0;
    INold = IN;
end
```



Proper Circuit Partition

 
- ◆ Partitioning large circuits into **unidirectional** blocks
 - Easy to derive closed-form equations of each block for quick evaluation



Avoid Time Integration

- ◆ Ex: Single-slope ADC
 - Combining analog blocks to form 2 unidirectional modules
 - Tracking + ramping
 - Closed form equations:

 
$$V_{out} = \beta t + \beta RC \left(e^{-\frac{t}{RC}} - 1 \right) + \alpha \left(1 - e^{-\frac{t}{RC}} \right) + V_0 e^{-\frac{t}{RC}}$$



Ref: S. Liao and M. Horowitz, "A Verilog piecewise-linear analog behavior model for mixed-signal validation," IEEE TCAS-I, vol. 61, no. 8, pp. 2229–2235, Aug. 2014.

Reshape Model Output

 - ◆ Ramp response appears very often in digital circuits
 - Not reasonable for analog models
- ◆ A gate keeper is often required to “smooth” the sharp output signals




Ref: S. Liao and M. Horowitz, “A Verilog piecewise-linear analog behavior model for mixed-signal validation,” IEEE TCAS-I, vol. 61, no. 8, pp. 2229–2235, Aug. 2014.

Timing Models

- ◆ Digital simulation often use zero-delay mode for functional validation
 - However, timing information (rise/fall/delay) is important to analog circuits
- ◆ Calibration is required to fix the timing parameters

	Hspice	w/o timing model	With timing model
Lock frequency	800MHz	1000MHz	793MHz

 


Ref: J.-Y. Chen, S.-W. Wang, C.-H. Lin, C.-N. Liu, Y.-J. Lin, M.-J. Lee, Y.-L. Lo, S.-Y. Kao, “Automatic Behavioral Model Generator for Mixed-Signal Circuits Based on Structure Recognition and Auto-Calibration”, in Proc. Int’l SOC Design Conf., Nov. 2015

Interface Modeling

- ◆ According to the input/output types, different approaches are adopted to model the interface
 - Digital in & out
 - use standard Verilog input/output format
 - Analog in & out
 - model input/output signals as PWL form or
 - use real-value connection approaches
 - Digital ↔ Analog
 - use PWL waveform or direct connection
- ◆ Be careful about the **multi-driven** problem

PWL Waveforms as Input/Output

 - ◆ Determine the system output according to the transfer function for every input
- ◆ Set the evaluation period T based on the required accuracy
 - Calculate the output value for every T seconds



Ref: S. Liao and M. Horowitz, "A Verilog piecewise-linear analog behavior model for mixed-signal validation," IEEE TCAS-I, vol. 61, no. 8, pp. 2229–2235, Aug. 2014.

Real Value Connection (1/2)

- ◆ Directly assign the real value from module A to module B --> skip the port connection

◆ Format : **Module_name . Real_value_name**

Module b

```
module inv(in,out);
input in;
output reg out;
real Vin,Vout;
parameter vdd=1.8,gnd=0.0;
always@(in)
begin
out=~in;
if(Vin>(0.5*vdd))
begin
Vout=gnd;
end
else
begin
Vout=vdd;
end
end
endmodule
```

Top Module

```
inv a(.in(in),.out(net));
inv b(.in(net),.out(out));
always @*
b.Vin = a.Vout;
endmodule
```

Module a

```
module inv(in,out);
input in;
output reg out;
real Vin,Vout;
parameter vdd=1.8,gnd=0.0;
always@(in)
begin
out=~in;
if(Vin>(0.5*vdd))
begin
Vout=gnd;
end
else
begin
Vout=vdd;
end
end
endmodule
```

Real Value Connection (2/2)

- ◆ Real values can be passed through ports in Verilog-AMS and latest version of Verilog → **wreal** type
 - **wreal** = wire + real value
 - Supported in Verilog-AMS and SystemVerilog 2012
- ◆ Used as normal wire variables → **only for I/O ports**
 - **real** type for internal variables

Passing real values
for those input ports


Internal variables use
reg and **real** types

```
module sdm_rnm (Ain, clk_1mhz, reset_n, Dout);
input Ain, clk_1mhz, reset_n;
output Dout;
wreal Ain, dlay[2:1];
reg Dout;
real sdm_sign_val;
real sdm_sum1, real sdm_sum2;
```

Real-Valued Verilog Model (1/2)

◆ An example of continuous voltage/current values

```
`timescale 1us/100ps
module vin_pos_switch_tb();
// top-level signals and variables
wire gnd = 1'b0;
wire vin, vpos, cin, cout;
reg sample=1'b0, sel=1'b0;
real V_vin, V_vpos, V_cin, V_cout;
// sub-module instantiations
vsource #(.td(100)) Vin (.m(gnd), .p(vin));
vsource #(.td(100)) Vpos (.m(gnd), .p(vpos));
spdt_sel Sin(.o(cin), .i1(vin), .i0(vpos), .sel(sel));
capacitor Cap (.m(cout), .p(cin));
// sample-switch modeling
assign cout = (sample) ? gnd : 1'bz;
always @* V_vin = (sample) ? 0.0 : Cap.V_m;
always @* Cap.V_m = V_cout;
// connectivity for variables
always @* V_vin = Vin.V_p;
always @* Sin.V_i1 = V_vin;
always @* V_vpos = Vpos.V_p;
always @* Sin.V_i0 = V_vpos;
always @* V_cin = Sin.V_o;
always @* Cap.V_p = V_cin;
```

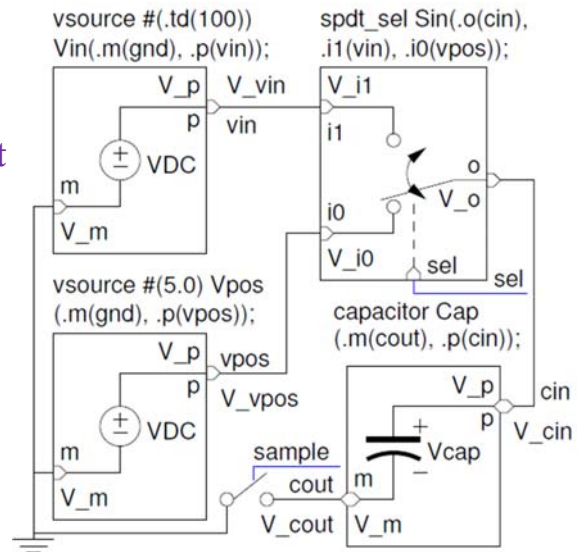


Assign real type variable

Ref: C.Wenger, "Method of Modeling Analog Circuits in Verilog for Mixed-signal Design Simulations," IEEE European Conf. on Circuit Theory and Design, 2013.

Real-Valued Verilog Model (2/2)

 
◆ Output waveform of continuous voltage/current



Ref: C.Wenger, "Method of Modeling Analog Circuits in Verilog for Mixed-signal Design Simulations," IEEE European Conf. on Circuit Theory and Design, 2013.

Multi-driven Problem of RVM

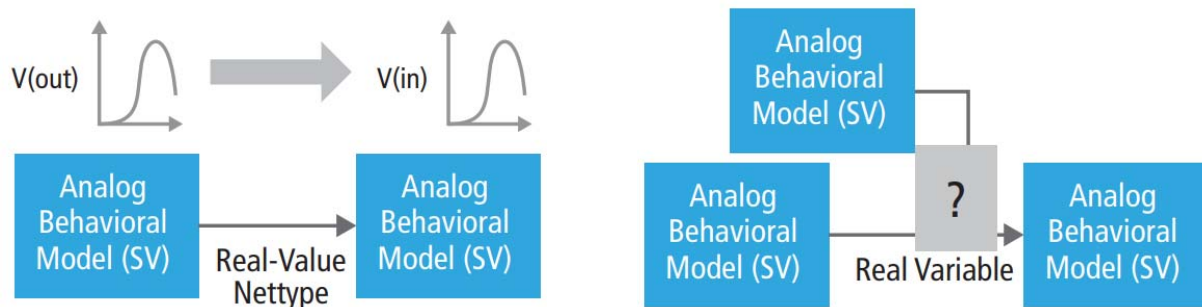- ◆ In legacy Verilog code
 - No bidirectional real number ports
 - Only one driver allowed on each port connection
 - No direct support for real valued signals
- ◆ In latest version SystemVerilog
 - Support Nettype and User-defined types (UDT)
 - Similar to structure in C → pack multiple variables




Outline

- ◆ Introduction
- ◆ Real-Valued Behavioral Models in Verilog
- ◆ **Portable Models for Verilog/Verilog-A**
- ◆ Test Results
- ◆ Conclusions

Portable Methodology Flow

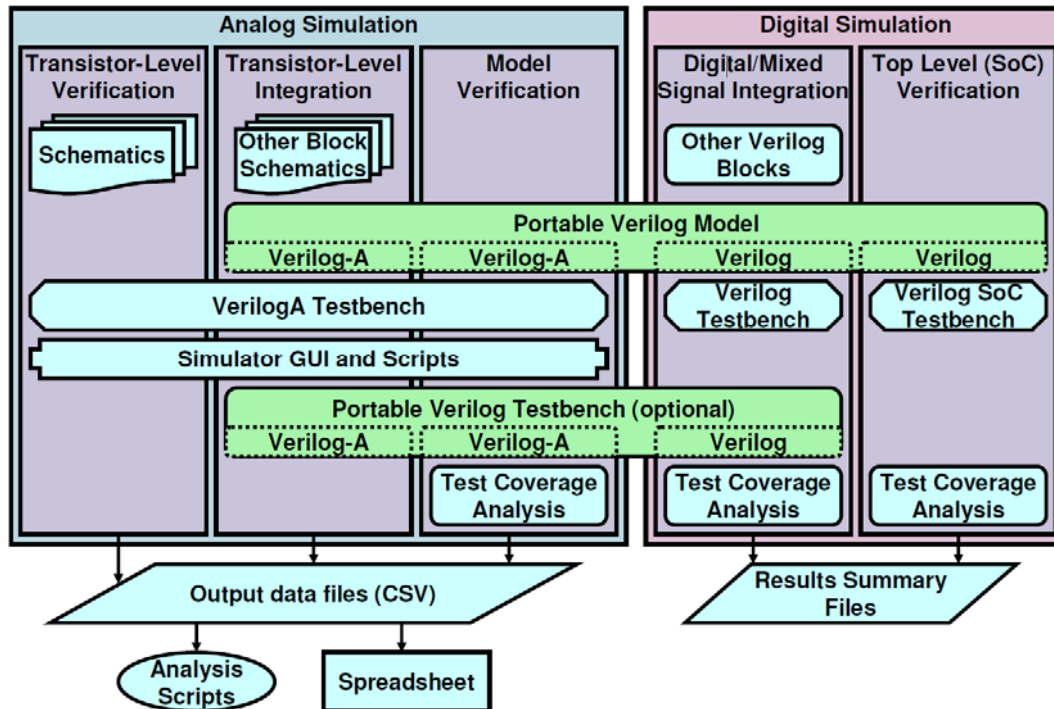- ◆ Create a common code that is portable to Verilog/A



Ref: Bill Ellersick, "Real Portable Models for System/Verilog/A/AMS", SNUG 2010.

P.27

Portable Methodology


- ◆ Use discrete-time features common to Verilog/A
 - Common code to manipulate reals and integers
 - Use powerful `define to write portable models

	Verilog	Verilog-A
Define Macro	<pre> `define AnalogInput wire real `define AnalogOutput real `define LogicInput wire `define LogicOutput wire </pre>	<pre> `define AnalogInput electrical `define AnalogOutput electrical `define LogicInput electrical `define LogicOutput electrical </pre>
Verilog/A code	<pre> `LogicInput [11:0] adcout; `AnalogInput aafout; `AnalogOutput ibg5u; `AnalogOutput adcinp; `LogicOutput adccclk; `LogicOutput rstn; wire [11:0] adcout; real aafout; wire real ibg5u; wire real adcinp; wire adccclk; wire rstn; </pre>	<pre> electrical [11:0] adcout; electrical aafout; electrical ibg5u; electrical adcinp; electrical adccclk; electrical rstn; </pre>

Ref: Bill Ellersick, "Real Portable Models for System/Verilog/A/AMS", SNUG 2010.

Verilog v.s. Verilog-A

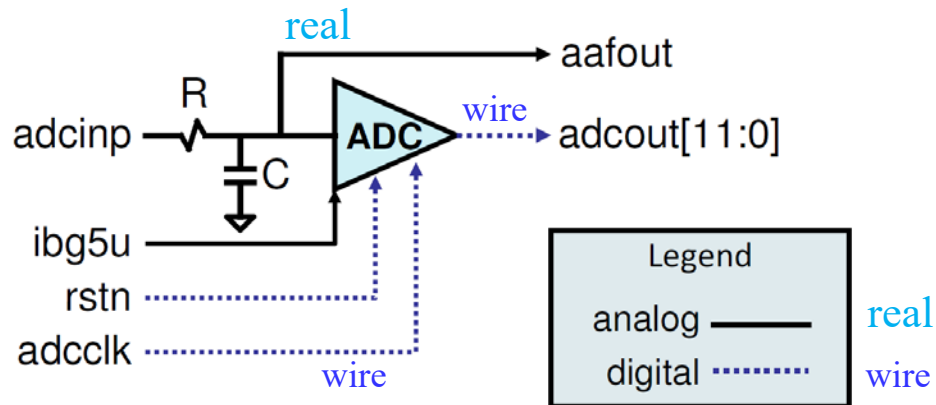- ◆ Both Verilog and Verilog-A support:
 - Couple real or binary values in and out of module ports
 - Specify when to update values
 - Equations to update real and integer values
- ◆ Example : ADC with RC filter



Ref: Bill Ellersick, "Real Portable Models for System/Verilog/A/AMS", SNUG 2010.


adcX (Input/Output Declarations)

Verilog

```
wire [11:0] adcout;  
real aafout;  
wire real ibg5u;  
wire real adcinp;  
wire adcclock;  
wire rstn;
```

Verilog-A
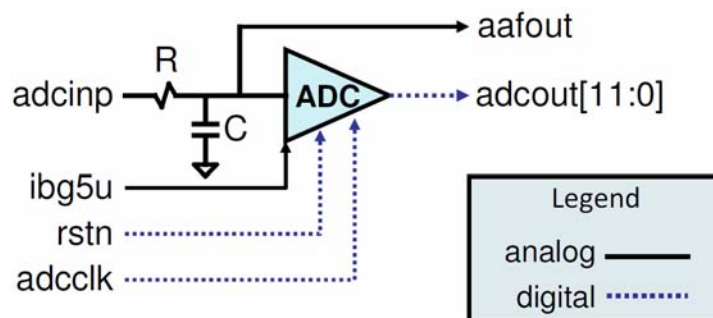
```
electrical [11:0] adcout;  
electrical aafout;  
electrical ibg5u;  
electrical adcinp;  
electrical adcclock;  
electrical rstn;
```



Ref: Bill Ellersick, "Real Portable Models for System/Verilog/A/AMS", SNUG 2010.

adcX (RC Filter)

Verilog

```
initial #1e-10 forever begin           // evaluate ~10 times highest freq
    ires = (adcinp - aafout_v) / Raaf;    // resistor current
        // capacitor difference equation  $C = V + I * \text{deltaT} / C$ 
    aafout_v = aafout_v + ires * ($realtime-lsttim) / Caaf;
    lsttim = $realtime;                   // save time
#1e-10; end
```

Verilog-A

```
@(timer(1e-10,1e-10)) begin           // evaluate ~10 times highest freq
    ires = (V(adcinp) - aafout_v) / Raaf; // resistor current
        // capacitor difference equation  $C = V + I * \text{deltaT} / C$ 
    aafout_v = aafout_v + ires * ($realtime-lsttim) / Caaf;
    lsttim = $realtime;                   // save time
end
```

adcX (Excerpts)

Verilog

```
always @(posedge adcclk or negedge rstn) begin
    if(!rstn) begin
        for(i=11; i>0; i=i-1) int[i] = 0;
        $display("adcX reset at %10.4g\n", $realtime);
    end else begin
        refv0 = 0.5 * ibg5u/5e-6;
        refv = refv0; // start with full
        vadc = adcinp-Voff+refv0; // sample input, s
        for(i=11; i>0; i=i-1) begin
            if(vadc > refv) begin
                adcout_int[i] = 1; // out
                vadc = vadc - refv; // and
            end else begin
                adcout_int[i] = 0; // else
            end
            refv = refv / 2.0; // halve
        end
    end
end
```

Verilog-A

```
@(cross(V(adcclk)-(vdd_v+vss_v)/2.0, 1)
    or cross(V(rstn)-(vdd_v+vss_v)/2.0, -1)) begin
    if(!(V(rstn)>(vdd_v+vss_v)/2.0) ? 1 : 0) begin
        generate i(11,0) adcout_int[i] = 0;
        $display("adcX reset at %10.4g\n", $realtime);
    end else begin
        refv0 = 0.5 * I(ibg5u)/5e-6;
        refv = refv0; // start with full
        vadc = V(adcinp)-Voff+refv0; // sample input, su
        generate i(11,0) begin
            if(vadc > refv) begin
                adcout_int[i] = 1; // output logic hig
                vadc = vadc - refv; // and subtract ref
            end else begin
                adcout_int[i] = 0; // else output logi
            end
            refv = refv / 2.0; // halve refv for n
        end
    end
end
```

adcX(Assignments)

```
assign adcout[0] = adcout_int[0];
assign adcout[1] = adcout_int[1];
assign adcout[2] = adcout_int[2];
assign adcout[3] = adcout_int[3];
assign adcout[4] = adcout_int[4];
assign adcout[5] = adcout_int[5];
assign adcout[6] = adcout_int[6];
assign adcout[7] = adcout_int[7];
assign adcout[8] = adcout_int[8];
assign adcout[9] = adcout_int[9];
assign adcout[10] = adcout_int[10];
assign adcout[11] = adcout_int[11];
always @( aafout_v) aafout = aafo
```

Verilog

Verilog-A

```
adcout[0] <+ transition((adcout_int[0] ? vdd_v : vss_v), 100e-12, 100e-12);
adcout[1] <+ transition((adcout_int[1] ? vdd_v : vss_v), 100e-12, 100e-12);
adcout[2] <+ transition((adcout_int[2] ? vdd_v : vss_v), 100e-12, 100e-12);
adcout[3] <+ transition((adcout_int[3] ? vdd_v : vss_v), 100e-12, 100e-12);
adcout[4] <+ transition((adcout_int[4] ? vdd_v : vss_v), 100e-12, 100e-12);
adcout[5] <+ transition((adcout_int[5] ? vdd_v : vss_v), 100e-12, 100e-12);
adcout[6] <+ transition((adcout_int[6] ? vdd_v : vss_v), 100e-12, 100e-12);
adcout[7] <+ transition((adcout_int[7] ? vdd_v : vss_v), 100e-12, 100e-12);
adcout[8] <+ transition((adcout_int[8] ? vdd_v : vss_v), 100e-12, 100e-12);
adcout[9] <+ transition((adcout_int[9] ? vdd_v : vss_v), 100e-12, 100e-12);
adcout[10] <+ transition((adcout_int[10] ? vdd_v : vss_v), 100e-12, 100e-12);
adcout[11] <+ transition((adcout_int[11] ? vdd_v : vss_v), 100e-12, 100e-12);
V(aafout) <+ aafout_v;
V(ibg5u) <+ 1.1; // voltage termination at current input
```


EDA-LAB

P.33



Outline

- ◆ Introduction
- ◆ Real-Valued Behavioral Models in Verilog
- ◆ Portable Models for Verilog/Verilog-A
- ◆ **Test Results**
- ◆ Conclusions

Phase Locked Loop (PLL) Model

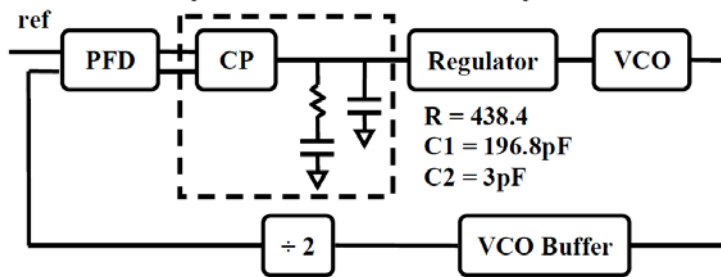


Circuit	Spectre	Verilog
PLL	33min 48s	4.4s

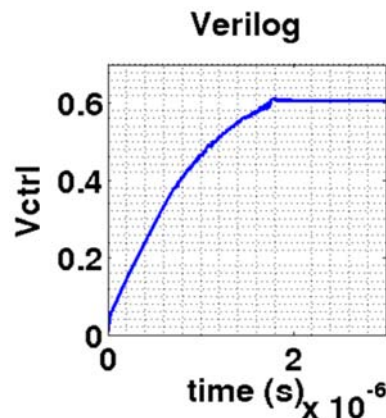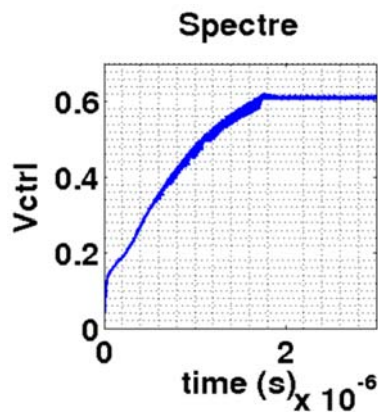



Ref: S. Liao and M. Horowitz, "A Verilog piecewise-linear analog behavior model for mixed-signal validation," IEEE TCAS-I, vol. 61, no. 8, pp. 2229–2235, Aug. 2014.

Buck Converter Model

 


Circuit	Spectre	Verilog
Buck	25h 15min	0.46s

Rload change at 1.5us
from 20 Ω to 10 Ω

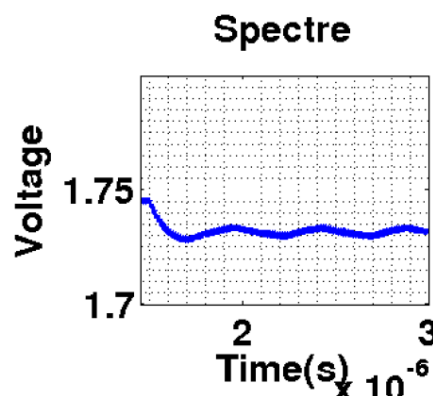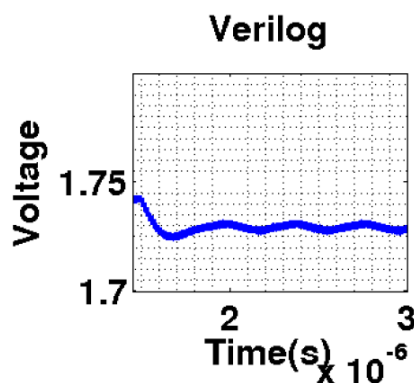

Ref: S. Liao and M. Horowitz, "A Verilog piecewise-linear analog behavior model for mixed-signal validation," IEEE TCAS-I, vol. 61, no. 8, pp. 2229–2235, Aug. 2014.

D/A Converter Model

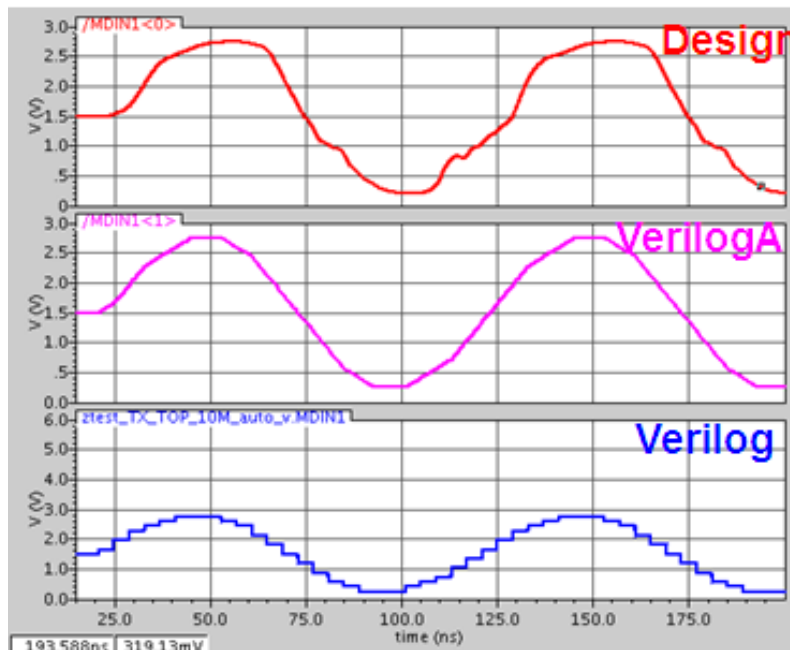

Spectre 7m 23.5s

Verilog-A 17.0s

Verilog 16.4s


- ◆ Verilog-A waveform is more smooth
→ high accuracy
- ◆ Beh. models do provide great speedup

Ref: Y.-J. Lin, M.-J. Lee, Y.-L. Lo, S.-Y. Kao, "Automatic Mixed-Signal Behavioral Model Generation Environment", IEEE Int'l Symp. on VLSI Design, Automation, and Test, Apr. 2016. (Invited Paper)

PLL Model in Different Language

	Run Time (5us)	Correlation with Hspice
Full Spice	9.5 hours	1
Fast Spice	1.5 hours	99.9%
Verilog-A	1 minute	98.8%
System-Verilog	1 second	97.6%

 - ◆ Model PLL circuits based on PWC (piece-wise constant) real numbers and lookup tables
- ◆ Super fast with good accuracy !!



Ref: A. Lotfy, S. F. S. Farooq, Q. S. Wang, A. Yaldiz, P. Mosalikanti, N. Kurd, "A System-Verilog Behavioral Model for PLLs for Pre-Silicon Validation and Top-Down Design Methodology," IEEE Custom Integrated Circuits Conf. (CICC), Sep. 2015.

Conclusions

- ◆ A good behavioral model considers both accuracy and simulation speed
- ◆ Verilog-A models are good to provide high accuracy with various operators
 - Speedup is limited due to extra communication between analog/digital simulators
- ◆ Verilog models provide another choice to further improve simulation speedup
 - Accuracy may be sacrificed due to language limitation
- ◆ Choose different models at different applications
 - Portable behavioral models are convenient to be switched