



Logic Synthesis – Part 1

Technology-Independent Optimization

Prof. Chien-Nan Liu
Institute of Electronics
National Chiao-Tung Univ.

Tel: (03)5712121 ext:31211
E-mail: jimmyliu@nctu.edu.tw
<http://www.ee.ncu.edu.tw/~jimmy>

Courtesy: Prof. Jing-Yang Jou

NCTU MSEDALab.



1

Outline

- Synthesis overview
- RTL synthesis
- Two-level logic optimization
- Multi-level logic optimization
- Technology mapping
- Timing analysis
- Timing optimization
- Synthesis for low power

NCTU MSEDALab.




2

HDL Synthesis


- **Logic synthesis** programs transform Boolean expressions or **register-transfer level (RTL)** description (in Verilog/VHDL/C) into logic gate networks (netlist) in a particular library.
- Advantages
 - Reduce time to generate netlists
 - Easier to retarget designs from one technology to another
 - Reduce debugging effort
- Requirement
 - **Robust** HDL synthesizers

Synthesis Procedure

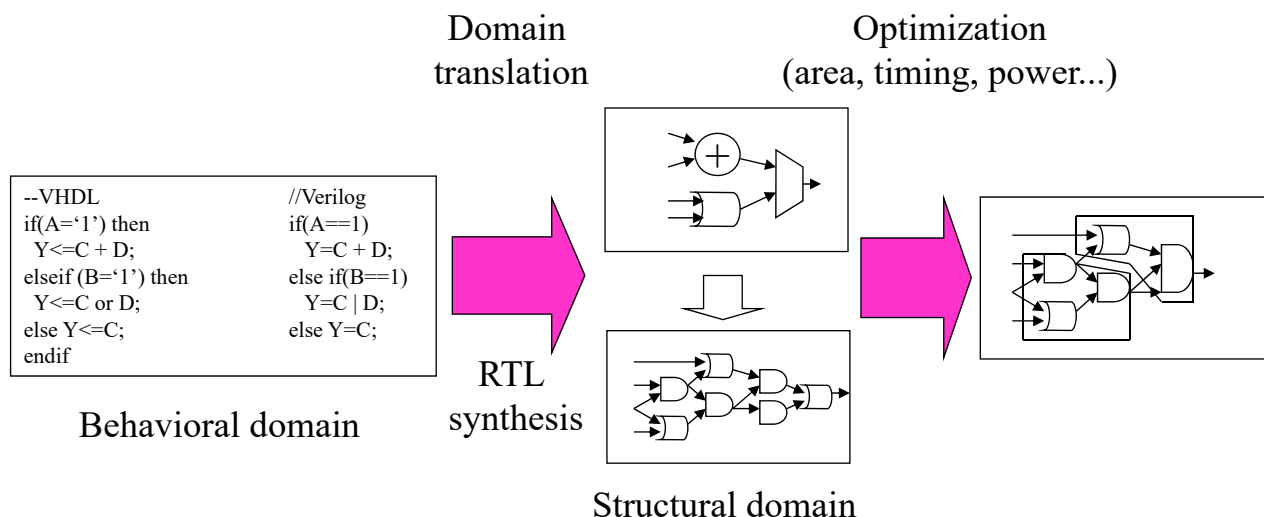
Synthesis = Domain Translation + Optimization



Domain Translation

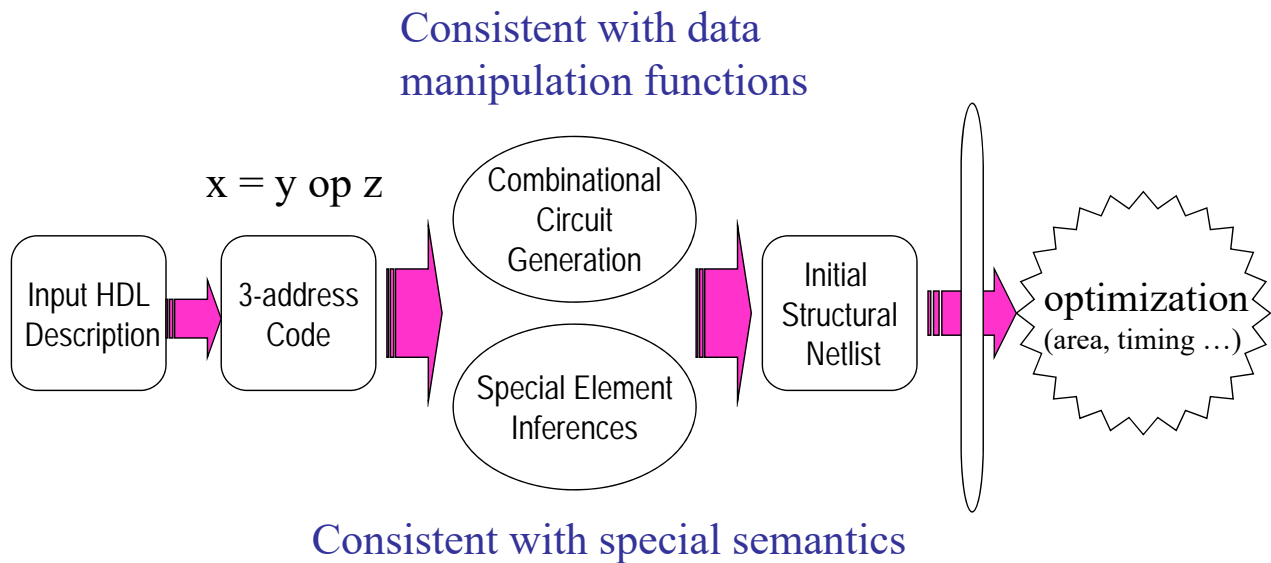

Optimization

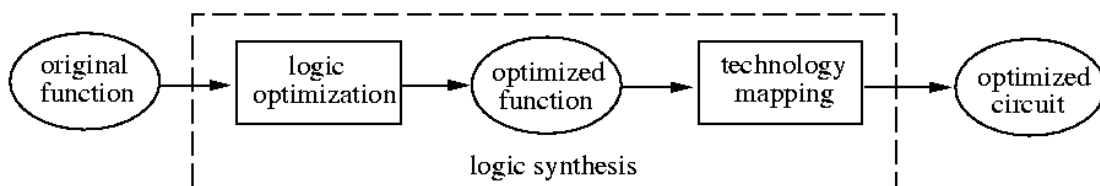

- **Technology-independent** optimization: **logic optimization**
 - Work on Boolean expression equivalent
 - Estimate size based on # of literals
 - Use simple delay models
- **Technology-dependent** optimization: **technology mapping/library binding**
 - Map Boolean expressions into a particular cell library
 - May perform some optimizations in addition to simple mapping
 - Use more accurate delay models based on cell structures


Technology-Independent Logic Optimization

- **Two-level:** minimize the # of product terms.

– $F = \bar{x}_1\bar{x}_2\bar{x}_3 + \bar{x}_1\bar{x}_2x_3 + x_1\bar{x}_2\bar{x}_3 + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3 \Rightarrow F = \bar{x}_2 + x_1\bar{x}_3.$

- **Multi-level:** minimize the #'s of literals, variables.

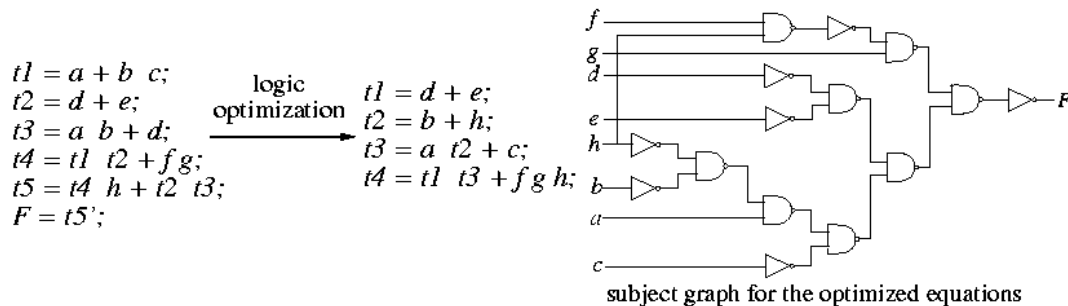– E.g., equations are optimized using a smaller number of literals.




- Methods/CAD tools: Quine-McCluskey method (exponential-time exact algorithm), Espresso (heuristics for two-level logic), MIS (heuristics for multi-level logic), Synopsys, etc.

Technology Mapping


- Goal: translation of a technology independent representation (e.g. Boolean networks) of a circuit into a circuit in a given technology (e.g. standard cells) with optimal cost
- Optimization criteria:
 - Minimum area
 - Minimum delay
 - Meeting specified timing constraints
 - Meeting specified timing constraints with minimum area
- Usage:
 - Technology mapping after technology independent logic optimization
 - Technology translation

Standard Cells for Design Implementation

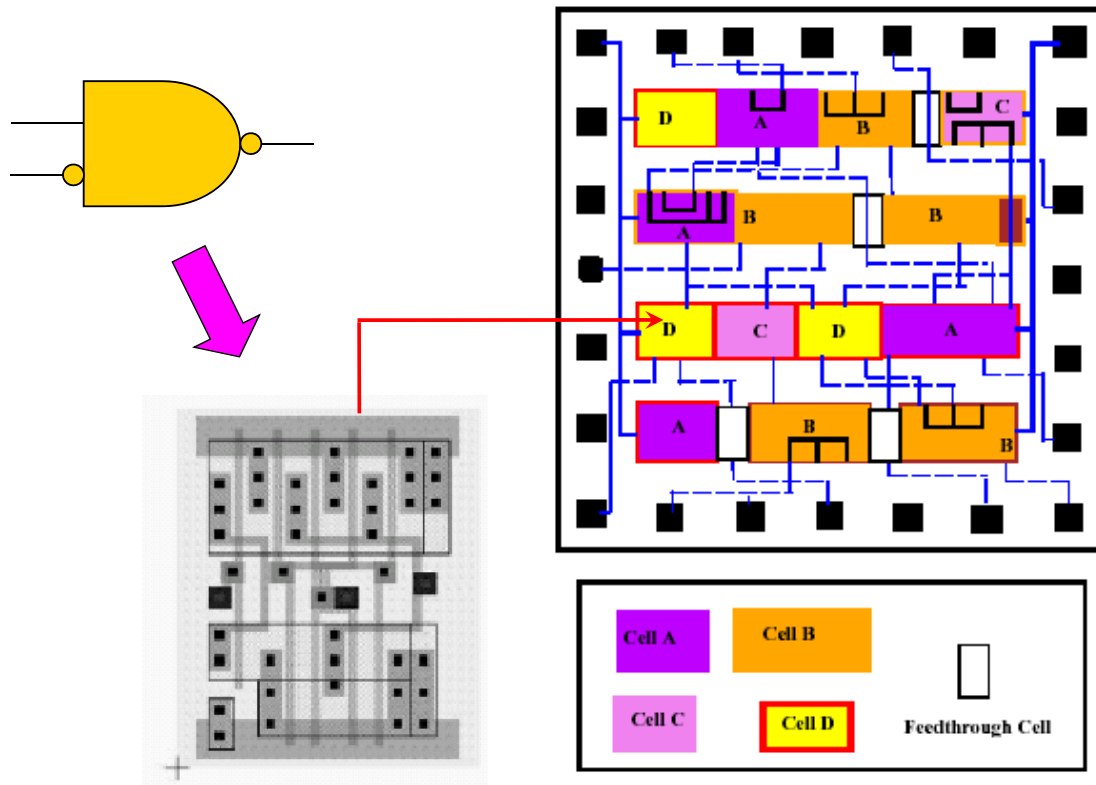

Timing Optimization

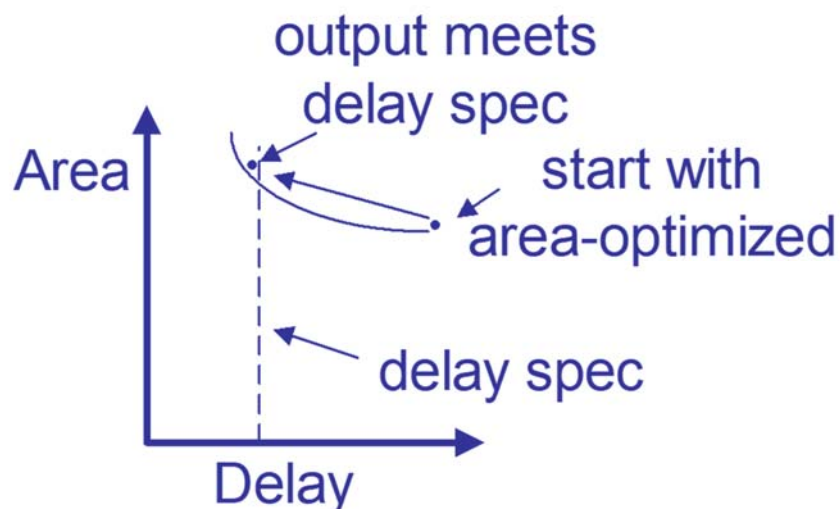- There is always a trade-off between area and delay
- Optimize timing to meet delay spec. with minimum area




Outline

- Synthesis overview
- **RTL synthesis**
 - Combinational circuit generation
 - Special element inferences
- Two-level logic optimization
- Multi-level logic optimization
- Technology mapping
- Timing analysis
- Timing optimization
- Synthesis for low power



Typical Domain Translation Flow

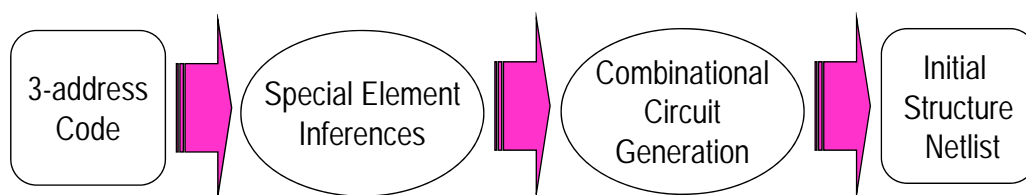- Translate original HDL code into 3-address format
- Conduct special element inferences before combinational circuit generation
- Conduct special element inferences process by process (local view)



Combinational Circuit Generation

- Functional unit allocation
 - Straightforward mapping with 3-address code
- Interconnection binding
 - Using control/data flow analysis

Functional Unit Allocation


- 3-address code
 - $x = y \text{ op } z$ in general form
 - Function unit op with inputs y and z and output x

$x=c+d+e;$
 $\text{if}(a==b) \ x= e-f;$
 $y=x;$

3-address code

$t=c+d;$
 $x=t+e;$
 $s = (a==b);$
 $\text{if}(s) \ x= e-f;$
 $y=x;$

Implicit multiplexer

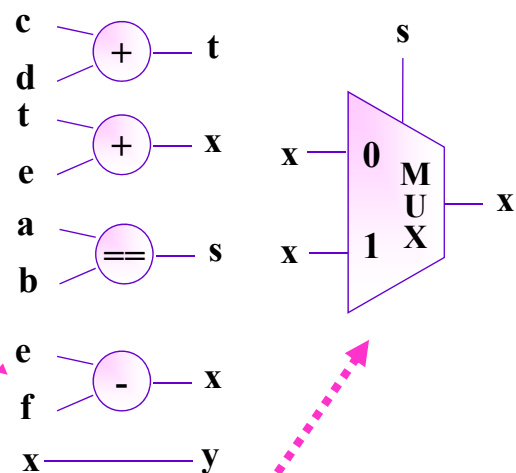



Interconnection Binding

- Need the dependency information among functional units
 - Using **control/data flow analysis**
 - A traditional technique used in compiler design for a variety of code optimizations
 - Statically analyze and compute the set of assignments reaching a particular point in a program

Control/Data Flow Analysis

- Terminology
 - A **definition** of a variable x
 - An assignment assigns a value to the variable x
 - $d1$ can reach $d4$ but cannot reach $d3$
 - $d1$ is killed by $d2$ before reaching $d3$
- A definition can only be affected by those definitions being able to reach it
- Use a set of data flow equations to compute which assignments can reach a target assignment
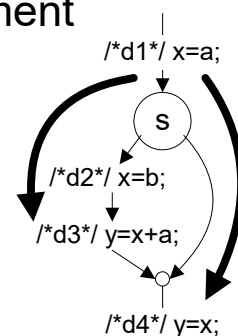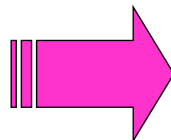
```
/*d1*/ x = a;  
    if(s) begin  
/*d2*/   x = b;  
/*d3*/   y = x + a;  
    end  
/*d4*/ y = x;
```



Combinational Circuit Generation: An Example

always @ (x or a or b or c or d or s)
begin
/*d1*/ x = a + b;
/*d2*/ if (s) x = c - d;
/*d3*/ else x = x;
/*d4*/ y = x;
end

Input HDL

always @ (x or a or b or c or d or s)
begin
/*d1*/ x = a + b;
/*d2*/ if (s) x = c - d;
/*d3*/ else x = x;
/*d4*/ x = s mux x;
/*d5*/ y = x;
end

Modified 3-address code

In[d1]={d4, d5} → computed by control/
data flow analysis
a → d1 (+) → x
b →

In[d2]={d1, d5}
c → d2 (-) → x
d →


In[d3]={*d1, d5}
x → d3 (wire) → x

In[d4]={*d2, *d3, d5}
s → d4 (1 d4 Mux) → x
x →


In[d5]={*d4, d5}

x → d5 (wire) → y

computed by control/
data flow analysis

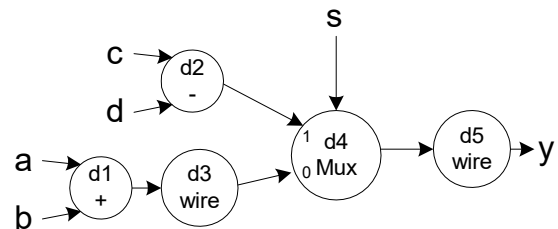

Interconnection binding

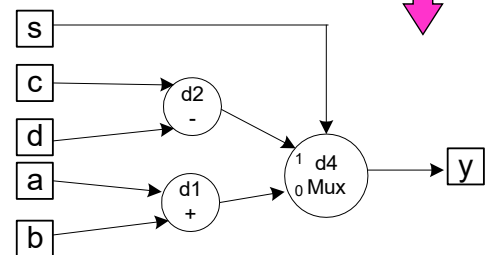

Final result

Functional unit allocation



Outline

- Synthesis overview
- RTL synthesis
 - Combinational circuit generation
 - **Special element inferences**
- Two-level logic optimization
- Multi-level logic optimization
- Technology mapping
- Timing analysis
- Timing optimization
- Synthesis for low power



Special Element Inferences

- Given a HDL code at RTL, three special elements need to be inferred to keep the special semantics
 - Latch (D-type) inference
 - Flip-Flop (D-type) inference
 - Tri-state buffer inference
- Some simple rules are used in typical approaches

```
reg Q;  
always@(D or en)  
  if(en) Q = D;
```

Latch inferred!!

```
reg Q;  
always@(posedge clk)  
  Q = D;
```

Flip-flop inferred!!

```
reg Q;  
always@(D or en)  
  if(en) Q = D;  
  else  Q = 1'bz;
```

**Tri-state buffer
inferred!!**



Preliminaries

- Sequential section
 - Edge triggered always statement
- Combinational section
 - All signals whose values are used in the always statement are included in the sensitivity list

```
reg Q;  
always@(posedge clk)  
  Q = D;
```

Sequential section
Conduct flip-flop inference

```
reg Q;  
always@(in or en)  
  if(en) Q=in;
```

Combinational section
Conduct latch inference



Typical Latch Inference

- Conditional assignments are not completely specified
 - Check if the *else-clause* exists
 - Check if all case items exist
- Outputs conditionally assigned in an if-statement are not assigned before entering or after leaving the if-statement

```
always@(D or S)
if(S) Q = D;
```

└─→ Infer latch
for Q


```
always@(S or A or B)
begin
Q = A;
if(S) Q = B;
end
```

→ Do not infer
latch for Q




Terminology (1/2)

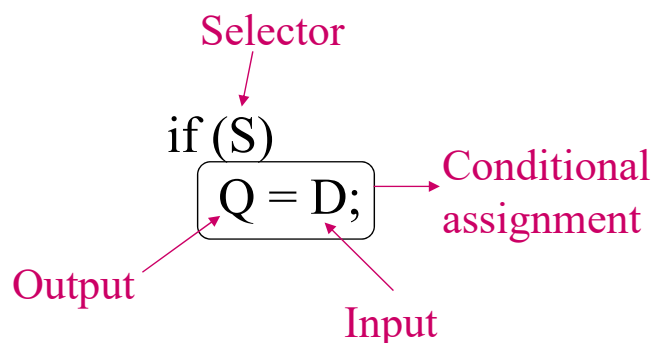- Conditional assignment
- Selector: S
- Input: D
- Output: Q




Terminology (2/2)

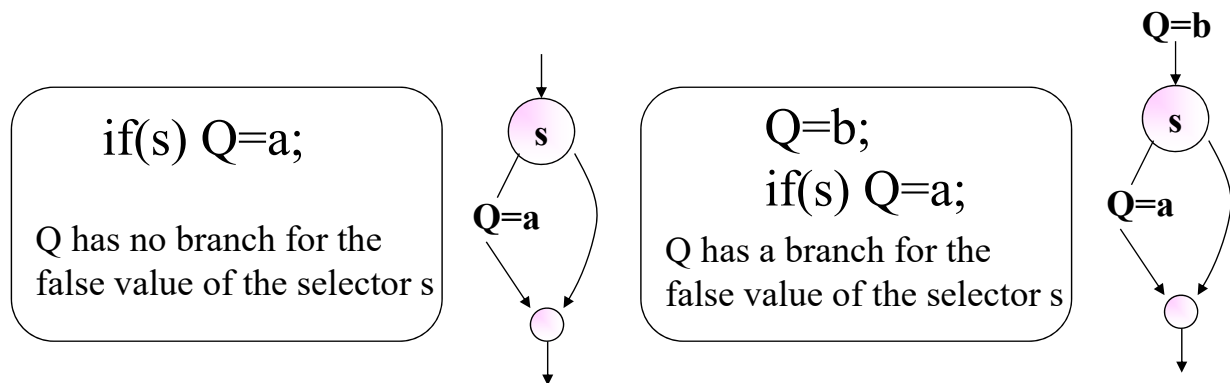- A variable Q has a *branch* for a value of selector s
 - The variable Q is assigned a value in a path going through the branch



Rules of Latch Inference (1/2)

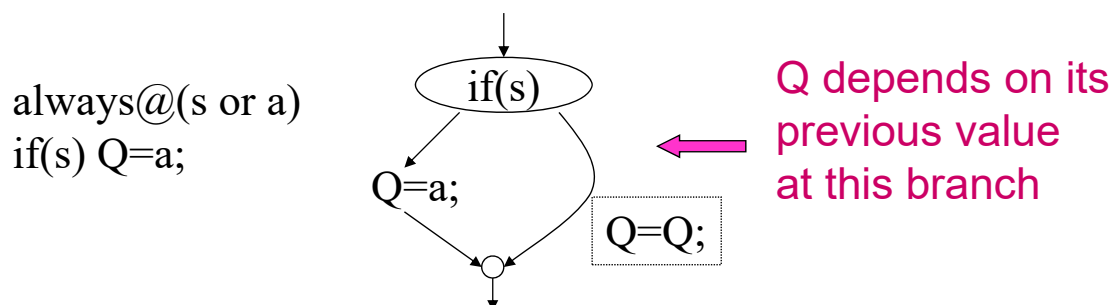
- Condition 1: There is no branch associated with the output of a conditional assignment for a value of the selector
 - Output depends on its previous value implicitly



Rules of Latch Inference (2/2)

- Condition 2: The output value of a conditional assignment depends on its previous value explicitly
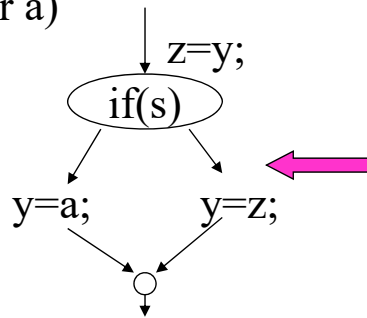
```
always@(s or z or y or a)
begin
  z = y;
  if(s) y=a;
  else y=z;
end
```




y depends on its previous value at this branch via the assignment z=y;

Terminology

- Clocked statement: edge-triggered always statement
 - Simple clocked statement
e.g., **always @ (posedge clock)**
 - Complex clocked statement
e.g., **always @ (posedge clock or posedge reset)**
- Flip-flop inference must be conducted only when synthesizing the **clocked statements**


Infer FF for Simple Clocked Statements (1/2)

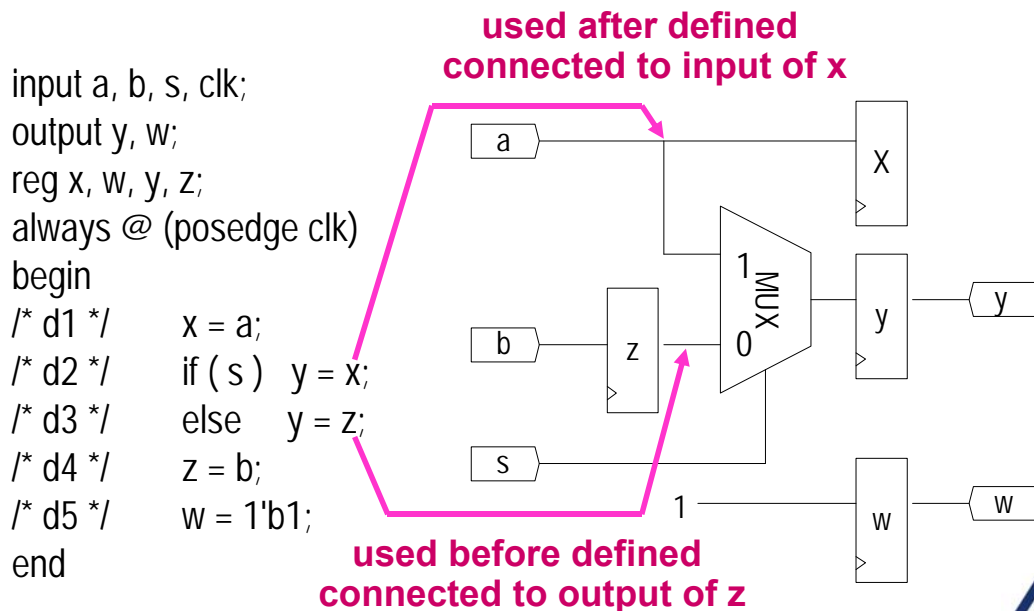- Infer a flip-flop for **each variable** being assigned in the simple clocked statement



Infer FF for Simple Clocked Statements (2/2)

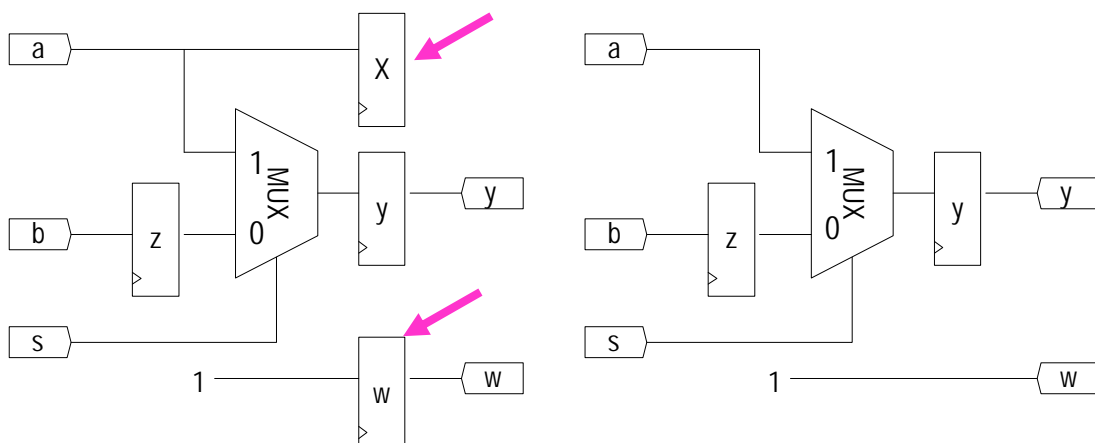- Two post-processes
 - Propagating constants
 - Removing the flip-flops without fanouts



Infer FF for Complex Clocked Statements

- The edge-triggered signal not used in the following operations is chosen as the clock signal
- The usage of asynchronous control pins requires the following syntactic template
 - An if-statement immediately follows the always statement
 - Each variable in the event list except the *clock signal* must be a selective signal of the if-statements
 - Assignments in the blocks B1 and B2 must be constant assignments (e.g., x=1, etc.)

always @ (posedge clock or posedge reset or negedge set)


if(reset) begin **B1** end
else if (!set) begin **B2** end
else begin **B3** end




Typical Tri-State Buffer Inference (1/2)

- If a data object Q is assigned a high impedance value 'Z' in a multi-way branch statement (if, case, ?:)
 - Associated Q with a tri-state buffer
- If Q associated with a tri-state buffer has also a memory attribute (latch, flip-flop)
 - Have the **Hi-Z propagation problem**
 - Real hardware cannot propagate Hi-Z value
 - Require two memory elements for the control and the data inputs of tri-state buffer
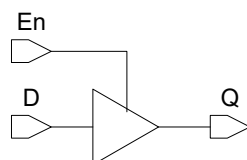
```
reg Q;  
always @ (En or D)  
if(En) Q = D;  
else Q = 1'bz;
```


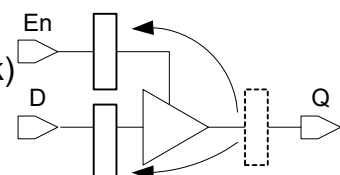
```
reg Q;  
always @ (posedge clk)  
if(En) Q = D;  
else Q = 1'bz;
```




Typical Tri-State Buffer Inference (2/2)

- It may suffer from mismatches between synthesis and simulation
 - Process by process
 - May incur the Hi-Z propagation problem

```
reg QA, QB;  
always @ (En or D)  
if(En) QA = D;  
else QA = 1'bz;
```
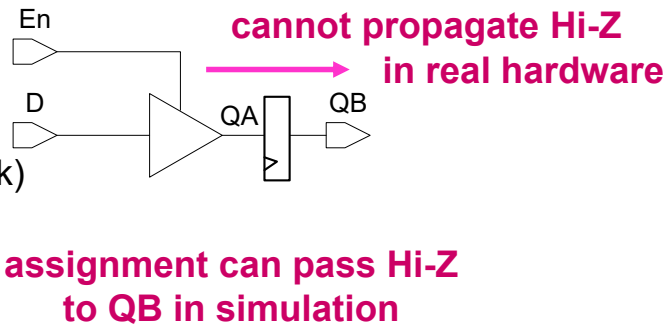
```
always @ (posedge clk)  
QB = QA;
```



Outline

- Synthesis overview
- RTL synthesis
- Two-level logic optimization
 - Basic logic operations
 - Exact minimization
 - Heuristic methods
- Multi-level logic optimization
- Technology mapping
- Timing analysis
- Timing optimization
- Synthesis for low power

Two-Level Logic Optimization

- Two-level logic optimization
 - Key technique in logic optimization
 - Many efficient algorithms to find a near minimal representation in a practical amount of time
 - In commercial use for several years
 - Minimization criteria: **number of product terms**
- Example: $F = XYZ + X\bar{Y}\bar{Z} + X\bar{Y}Z + \bar{X}YZ + XY\bar{Y}Z$



$$F = X\bar{Y} + YZ$$



Optimization Approach

- Exact Methods:
 - Compute minimum cover
 - Often impossible for large functions
 - Ex: Karnaugh maps, Quine-McCluskey
- Heuristic Methods:
 - Compute minimal covers (possibly minimum) in reasonable time
 - Large variety of methods and programs
 - Ex: MINI, PRESTO, ESPRESSO




Boolean Functions

- $B = \{0, 1\}$, $Y = \{0, 1, D\}$
- A Boolean function $f: B^m \rightarrow Y^n$
 - $f = \bar{x}_1 \bar{x}_2 + \bar{x}_1 \bar{x}_3 + \bar{x}_2 x_3 + x_1 x_2 + x_2 \bar{x}_3 + x_1 x_3$
- Input variables: x_1, x_2, \dots
- The value of the output partitions B^m into three sets
 - the on-set
 - the off-set
 - the dc-set (don't-care set)

Minterms and Cubes

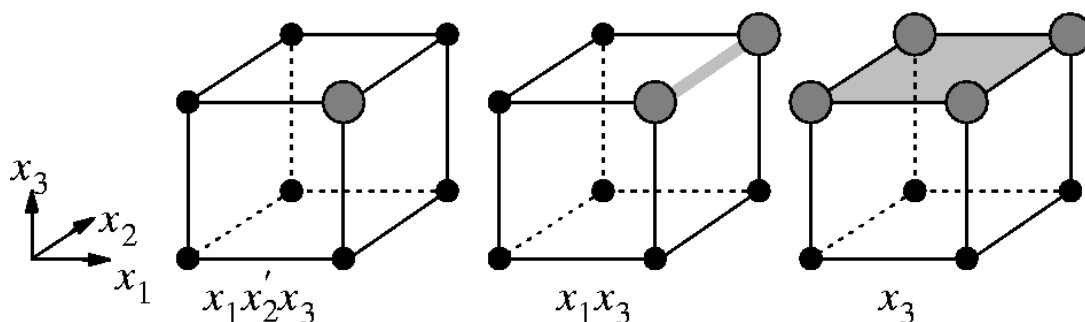- A **minterm** is a product of **all** input variables or their negations.
 - A minterm corresponds to a single point in B^n .
- A **cube** is a product of the input variables or their negations.
 - The fewer the number of variables in the product, the bigger the space covered by the cube.




Implicant and Cover

- An **implicant** is a cube whose points are either in the on-set or the dc-set.
- A **prime implicant** is an implicant that is not included in any other implicant.
- A set of prime implicants that together cover all points in the on-set (and some or all points of the dc-set) is called a prime cover.
- A prime cover is **irredundant** when none of its prime implicants can be removed from the cover.
- An irredundant prime cover is **minimal** when the cover has the minimal number of prime implicants.

Cover Examples

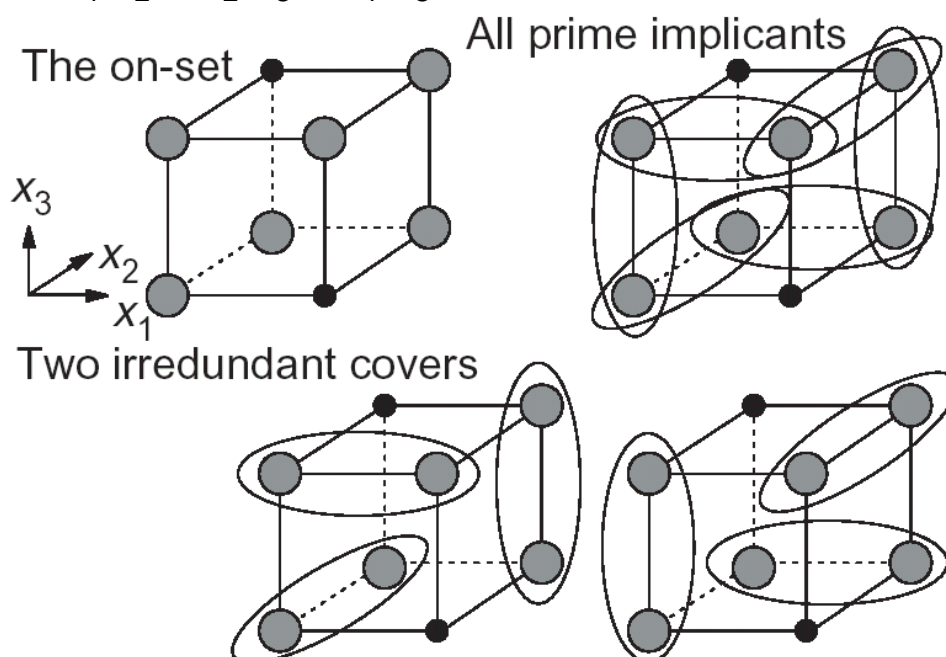- $f = \bar{x}_1 \bar{x}_3 + \bar{x}_2 x_3 + x_1 x_2$
- $f = \bar{x}_1 \bar{x}_2 + x_2 \bar{x}_3 + x_1 x_3$




The Positional-Cube Notation

- Encode each symbol by 2-bit fields as follows:

ϕ 00
 0 10
 1 01
 * 11

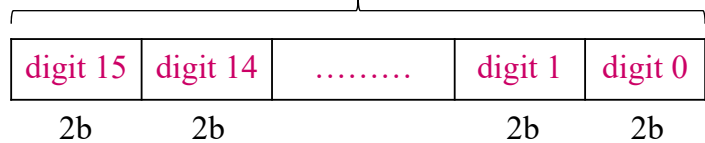One 32-bit integer \rightarrow 16 binary digits



- Example: $f = a'd' + a'b + ab' + ac'd$

10 11 11 10 ($a' - - d'$)
 10 01 11 11 ($a' b - -$)
 01 10 11 11 ($a b' - -$)
 01 11 10 01 ($a - c' d$)

- Example: $f_1 = a'b' + ab$; $f_2 = ab$; $f_3 = ab' + a'b$


10 10 1 0 0 ($a'b'$)
 10 01 0 0 1 ($a'b$)
 01 10 0 0 1 (ab')
 01 01 1 1 0 (ab)

$f_1 \rightarrow$
 $f_2 \uparrow$
 $f_3 \leftarrow$



AND Operation

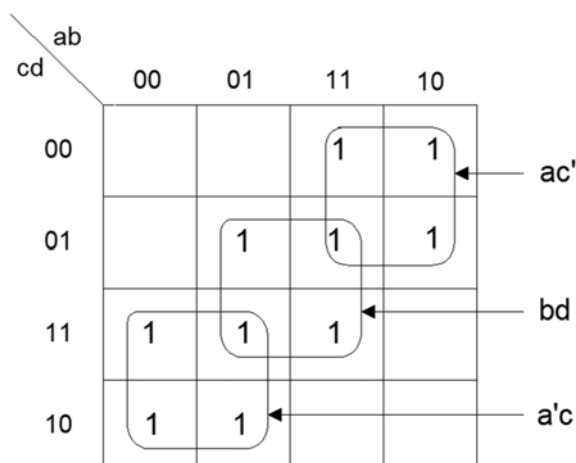Can be finished with a bit-wise AND instruction !!



10 11 01 11 $a'c$
 \cap 11 01 11 01 bd

 10 01 01 01 $a'bcd$

10 11 01 11 $a'c$
 \cap 01 11 10 11 ac'

 00 11 00 11 ϕ




Sharp Operation

$$\alpha \# \beta = \begin{array}{ccccc} a_1 b_1' & a_2 & \dots & a_{n-1} & a_n \\ a_1 & a_2 b_2' & \dots & a_{n-1} & a_n \\ \dots & \dots & \dots & \dots & \dots \\ a_1 & \dots & \dots & a_{n-1} b_{n-1}' & a_n \\ a_1 & \dots & \dots & a_{n-1} & a_n b_n' \end{array}$$

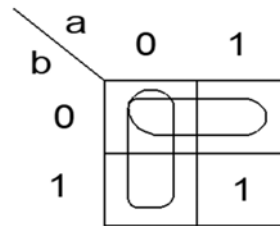• Example

$$11 \ 11 \# 01 \ 01 = \begin{array}{cc} 10 & 11 \\ 11 & 10 \end{array}$$




Disjoint Sharp Operation

$$\alpha \textcircled{\#} \beta = \begin{array}{ccccc} a_1 b_1' & a_2 & \dots & a_{n-1} & a_n \\ a_1 b_1 & a_2 b_2' & \dots & a_{n-1} & a_n \\ \dots & \dots & \dots & \dots & \dots \\ a_1 b_1 & a_2 b_2 & \dots & a_{n-1} b_{n-1}' & a_n \\ a_1 b_1 & a_2 b_2 & \dots & a_{n-1} b_{n-1} & a_n b_n' \end{array}$$

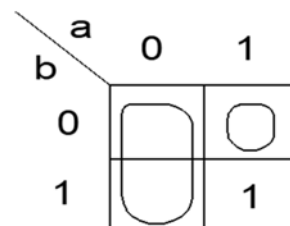• Example

$$11 \ 11 \textcircled{\#} 01 \ 01 = \begin{array}{cc} 10 & 11 \\ 01 & 10 \end{array}$$



Effects of Basic Logic Operations

- Consider each implicant as a set
- **Intersection** is the largest cube contained in both implicants and is computed by **AND operation**
- The **distance** between two implicants is the **number of empty fields in their intersection**
 - If there is any empty field, the two implicants are disjoint
- The **supercube** of two sets (the sum of two functions) can be obtained by union the sets (**bit-wise OR**)
 - The smallest cube containing both implicants
- The **(disjoint) sharp operation** can be used to compute the **complementation**

$$R = U \# (F^{ON} \cup F^{DC})$$



Cofactor (Restriction)

- Cofactor of f with respect to $x_i = 0$
 - $f_{x_i'} = f_{x_i=0} = f(x_1, x_2, \dots, x_i=0, \dots, x_n)$
- Cofactor of f with respect to $x_i = 1$
 - $f_{x_i} = f_{x_i=1} = f(x_1, x_2, \dots, x_i=1, \dots, x_n)$
 - Example:
$$f(x, y, z) = xy + yz' + x'z'$$
$$\rightarrow f_{x=0} = yz' + z' \quad f_{x=1} = y + yz'$$
- Cofactor with respect to any cube
 - Example:
$$f(x, y, z, w) = xy + zw' + w'x'$$
$$f_{x'y'} = f_{x=0, y=0} = zw' + w'$$
$$f_{xy'} = f_{x=1, y=0} = zw'$$



Cofactor of Implicants

- The cofactor of an implicant α w.r.t an implicant β is:

- $\alpha_\beta = \phi$ when α does not intersect β

Otherwise, $\alpha_\beta = a_1 + b_1' \quad a_2 + b_2' \quad \dots \quad a_n + b_n'$

- Example: Given $f = a'b' + ab$, calculate f_a

$$f = \begin{matrix} 10 & 10 \\ 01 & 01 \end{matrix} \quad \begin{matrix} c(a) = 01 & 11 \\ c(a') = 10 & 00 \end{matrix} \quad (\text{cube representation})$$

The cofactor of the first implicant is void

— $a'b'$ intersect with a is empty

The cofactor of the second implicant is $11 \ 01$

— $(01 \ 01) + (10 \ 00) = (11 \ 01)$

$\rightarrow f_a = b$



Shannon Expansion

$$\begin{aligned} f &= x' \cdot f_{x=0} + x \cdot f_{x=1} \\ &= x_i' \cdot y_j' \cdot f_{x_i' y_j'} + x_i \cdot y_j' \cdot f_{x_i y_j'} + x_i' \cdot y_j \cdot f_{x_i' y_j} + x_i \cdot y_j \cdot f_{x_i y_j} \end{aligned}$$

- Example:

$$f_x = y + zw'$$

$$f_{x'} = zw' + w'$$

$$f = x(y + zw') + x'(zw' + w')$$

- Decompose a function into two components, one for the subspace $x = 0$, the other for the subspace $x = 1$

$$f = x'f_{x'} + xf_x$$

- Allow a divide and conquer strategy on several problems
 - $f_{x'}$ and f_x do not depend on x and thus have one less variable



Consensus Operator

- Definition: $\forall x(f) = f_x \cdot f_{x'}$
- $\forall x(f)$ evaluate f to be true for $x = 1$ and $x = 0$
- Represent the component that is independent of that variable

- Example:

$$f(x,y,z,w) = xy + zw' + w'x'$$

$$f_x \cdot f_{x'} = zw' + w'y$$

Smoothing Operations

- Definition: $\exists x(f) = f_x + f_{x'}$
- $\exists x(f)$ evaluate f to be true when $x = 1$ or $x = 0$
- Example:

$$f(x,y,z,w) = xy + zw' + w'x'$$

$$\exists x(f) = f_x + f_{x'} = (zw' + w') + (zw' + y)$$

Boolean Difference

- $\frac{\partial f}{\partial x}$ is called Boolean difference of f with respect to x
- Definition: $\frac{\partial f}{\partial x} = f_x \oplus f_x^-$
- f is sensitive to the value of x when $\frac{\partial f}{\partial x} = 1$
- Example: $f(x,y,z,w) = xy + zw' + w'x'$
 $f_{x'} = f(x=0,y,z,w) = zw' + w'$
 $f_x = f(x=1,y,z,w) = y + zw'$
 $f_{x'} \oplus f_x = (zw' + w') \oplus (y + zw')$

Outline

- Synthesis overview
- RTL synthesis
- Two-level logic optimization
 - Basic logic operations
 - Exact minimization
 - Heuristic methods
- Multi-level logic optimization
- Technology mapping
- Timing analysis
- Timing optimization
- Synthesis for low power

The Quine-McCluskey Algorithm

- Theorem:[Quine,McCluskey] There exists a minimum cover for F that is prime
 - Need to look just at primes (reduces the search space)
- Classical methods: two-step process
 1. Generation of all prime implicants (of the union of the on-set and dc-set)
 2. Extraction of a minimum cover (covering problem)
- Exponential-time exact algorithm, huge amounts of memory!
- Other methods do not first enumerate all prime implicants; they use an implicit representation by means of ROBDDs.



Primary Implicant Generation (1/5)

ab		a			
		00	01	11	10
cd	00	X	1	0	1
	01	0	1	1	1
	11	0	X	X	0
	10	0	1	0	1

Diagram illustrating the Karnaugh map for Primary Implicant Generation (1/5). The map is a 4x4 grid with rows labeled 'cd' and columns labeled 'ab'. The grid is partitioned into four 2x2 quadrants by a vertical line labeled 'b' and a horizontal line labeled 'c'. The top-right quadrant is labeled 'd'. The cells contain values: X, 1, 0, 1, 0, 1, 1, 1, 0, X, X, 0, 0, 1, 0, 1. The 'X' values are located at (00,00), (11,11), and (11,10).



Primary Implicant Generation (2/5)

Implication Table		
	Column I	
zero "1"	0000	
one "1"	0100	
	1000	
	0101	
two "1"	0110	
	1001	
	1010	
	0111	
three "1"	1101	
	1111	
four "1"	1111	



Primary Implicant Generation (3/5)

Implication Table		
	Column I	Column II
	0000	0-00 -000
	0100	
	1000	010- 01-0
	0101	100- 10-0
	0110	
	1001	
	1010	01-1 -101
	0111	011- 1-01
	1101	
	1111	-111 11-1




Primary Implicant Generation (4/5)

Implication Table		
Column I	Column II	Column III
0000	0-00 *	01-- *
	-000 *	
0100		-1-1 *
1000	010-	
	01-0	
0101	100- *	
0110	10-0 *	
1001		
1010	01-1	
	-101	
0111	011-	
1101	1-01 *	
1111	-111	
	11-1	



Primary Implicant Generation (5/5)

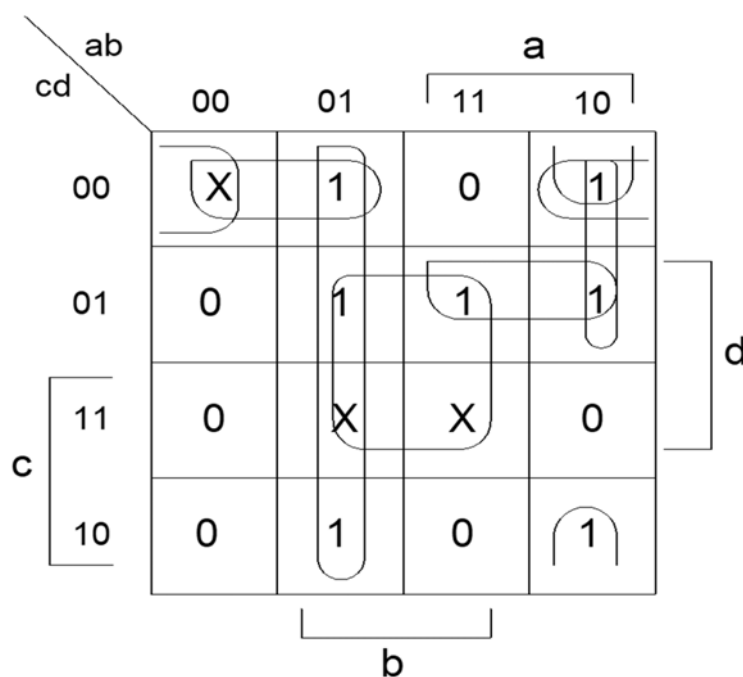

Prime Implicants:

$$0-00 = a'c'd'$$

$$100- = ab'c'$$

$$1-01 = ac'd$$

$$-1-1 = bd$$

$$-000 = b'c'd'$$

$$10-0 = ab'd'$$

$$01-- = a'b$$



Column Covering (1/4)

	4	5	6	8	9	10	13
0,4 (0-00)	×						
0,8 (-000)				×			
8,9 (100-)				×	×		
8,10 (10-0)				×		×	
9,13 (1-01)					×		×
4,5,6,7 (01- -)	×	×	×				
5,7,13,15 (-1-1)		×					×

rows = prime implicants

columns = ON-set elements

place an "X" if ON-set element
is covered by the prime implicant



Column Covering (2/4)

	4	5	6	8	9	10	13
0,4 (0-00)	×						
0,8 (-000)				×			
8,9 (100-)				×	×		
8,10 (10-0)				×		×	
9,13 (1-01)					×		×
4,5,6,7 (01- -)	×	×	×				
5,7,13,15 (-1-1)		×					×

If column has a single X, then the
implicant associated with the row
is essential. It must appear in
minimum cover



Column Covering (3/4)

	4	5	6	8	9	10	13
0,4 (0-00)	×						
0,8 (-000)				×			
8,9 (100-)				×	×		
8,10 (10-0)				×		×	
9,13 (1-01)					×		×
4,5,6,7 (01- -)	×	×	×				
5,7,13,15 (-1-1)		×					×

Eliminate all columns covered by essential primes



Column Covering (4/4)

	4	5	6	8	9	10	13
0,4 (0-00)	×						
0,8 (-000)				×			
8,9 (100-)				×	×		
8,10 (10-0)				×		×	
9,13 (1-01)					×		×
4,5,6,7 (01- -)	×	×	×				
5,7,13,15 (-1-1)		×					×

Find minimum set of rows that cover the remaining columns

$$f = ab'd' + ac'd + a'b$$



Petrick's Method

- Solve the **satisfiability** problem of the following function

$$P = (P1+P6)(P6+P7)P6(P2+P3+P4)(P3+P5)P4(P5+P7)=1$$

		4	5	6	8	9	10	13
P1	0,4 (0-00)	×						
P2	0,8 (-000)				×			
P3	8,9 (100-)				×	×		
P4	8,10 (10-0)				×		×	
P5	9,13 (1-01)					×		×
P6	4,5,6,7 (01- -)	×	×	×				
P7	5,7,13,15 (-1-1)		×					×

- Each term represents a corresponding column
- Each column must be chosen at least once
- All columns must be covered



ROBDDs and Satisfiability

- A Boolean function is **satisfiable** if an assignment to its variables exists for which the function becomes '1'
- Any Boolean function whose ROBDD is unequal to '0' is satisfiable.
- Suppose that choosing a Boolean variable x_i to be '1' costs c_i . Then, the **minimum-cost satisfiability** problem asks to minimize:
$$\sum_{i=1}^n c_i \mu(x_i)$$


where $\mu(x_i) = 1$ when $x_i = '1'$ and $\mu(x_i) = 0$ when $x_i = '0'$.

- Solving minimum-cost satisfiability amounts to computing the shortest path in an ROBDD, which can be solved in linear time.
 - Weights: $w(v, \eta(v)) = c_i$, $w(v, \lambda(v)) = 0$, variable $x_i = \phi(v)$.




Brute Force Technique

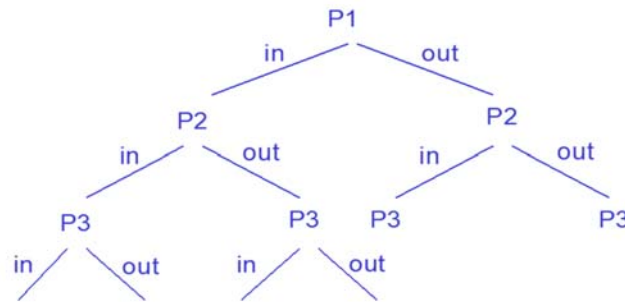- Brute force technique: Consider all possible elements



- Complete branching tree has $2^{|P|}$ leaves!!
 - Need to prune it
- Complexity reduction
 - Essential primes can be included right away
 - If there is a row with a singleton “1” for the column
 - Keep track of best solution seen so far
 - Classic **branch and bound**

Branch and Bound Algorithm

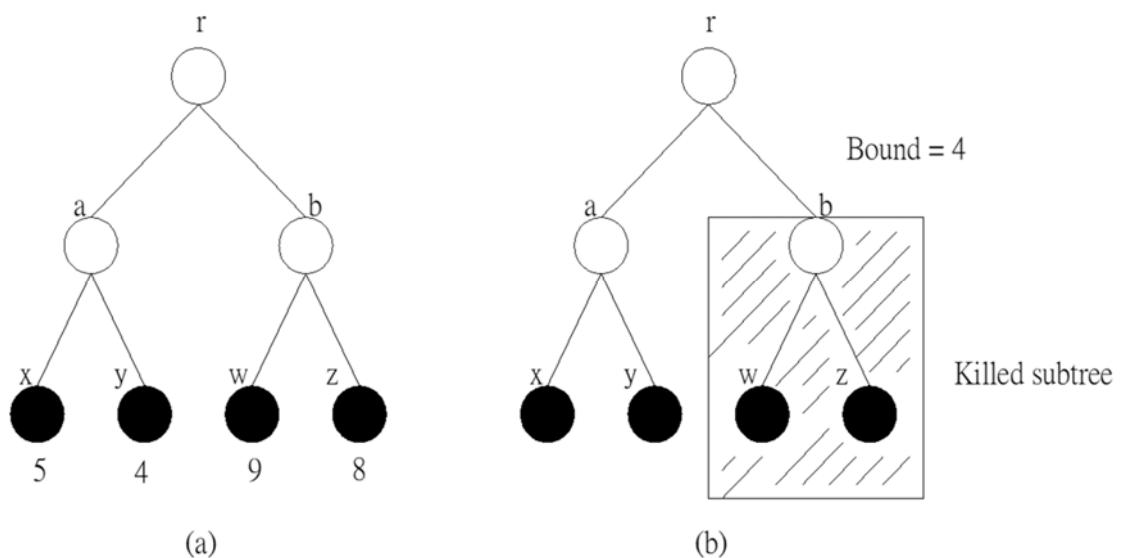

Outline

- Synthesis overview
- RTL synthesis
- Two-level logic optimization
 - Basic logic operations
 - Exact minimization
 - **Heuristic methods**
- Multi-level logic optimization
- Technology mapping
- Timing analysis
- Timing optimization
- Synthesis for low power



Why Heuristic Optimization ?


- Generation of **all** prime implicants is impractical
 - The number of prime implicants for functions with n variables is in the order of $3^n/n$
- Finding an *exact* minimum cover is NP-hard
 - Cannot be finished in polynomial time
- Heuristic method: provide irredundant covers with reasonably small cardinality
 - Fast and applicable to most functions
- Key idea: avoid generation of all prime implicants
 - Given initial cover
 - Make it prime
 - Make it irredundant
- Iterative improvement by modifying the implicants



Logic Minimizer -- ESPRESSO

- “ESPRESSO” developed by UC Berkeley
 - The kernel of existing synthesis tools
- EXPAND:
 - A minterm of $ON(f)$ is selected, and expanded until it becomes a prime implicant
 - Make implicants prime
- IRREDUNDANT COVER:
 - The prime implicant is put in the final cover, and all minterms covered by this prime implicant are removed
 - Make cover irredundant
- REDUCE:
 - Reduce size of each implicant while preserving cover
- Iteratively find alternative covers
 - Repeat the 3 steps to find the solutions with lower costs

ESPRESSO - Illustrated

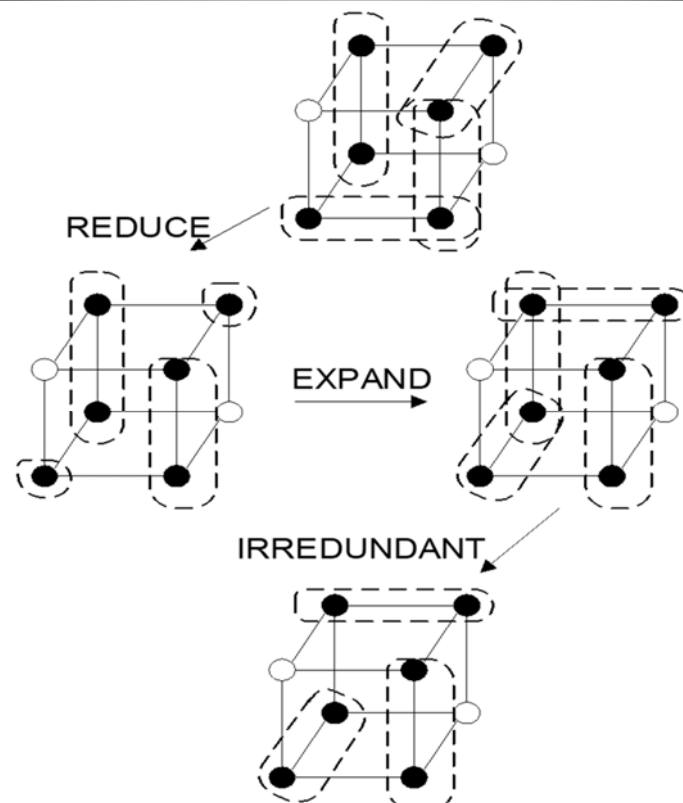

Pseudo Code of ESPRESSO

```
espresso (F, D)    /* F = ON_SET , D = DC_SET */
{
  R = complement (F + D);    /* R = OFF_SET */
  F = expand (F, R);          /* initial expansion */
  F = irredundant_cover (F, D); /* initial irredundant cover */
  E = essential_primes (F, D); /* extract essential primes */
  C = F - E;
  D = D + E;
  repeat {
    C = reduce (C, D);
    C = expand (C, R);
    C = irredundant_cover (C, D);
  } until (C unchanged);
  return C + E ;
}
```



Expand (1/3)

- Increase the size of each implicant
 - Implicants of smaller size can be covered and deleted
 - Maximally expanded implicants are primes
 - Raising one (or more) of its 0s to 1
- Validity checking
 - Checking for an intersection of the expanded implicant with F^{OFF}
- Two factors affect the quality and the efficiency of the algorithm
 - The order in which the implicants are selected
 - The order in which the 0 entries are raised to 1



Expand (2/3)

- Heuristic on the order of implicants
 - Compute column count vector (number of '1' in each column)
 - The weight of each cube is the inner product of itself and the column count vector
 - Sort implicants in **ascending** order of weight
 - Low weight correlates to having few 1s in the columns
 - **Expand first those cubes that are unlikely to be covered**
- Ex: $f = a'b'c' + ab'c' + a'bc' + a'b'c$; don't care : abc'

choose lowest weight →

F_{ON}:

10	10	10
01	10	10
10	01	10
10	10	01

column count →

31	31	31
----	----	----

F_{DC}:

01	01	10
01	11	01
11	01	01

F_{OFF}:

Column count vector = $[313131]^T$

Weight of the implicants = $(9,7,7,7)$

Ex: 2nd implicant of F_{ON}



01	10	10
x) 31	31	31
01	30	30

2nd weight = $0+1+3+0+3+0 = 7$



Expand (3/3)

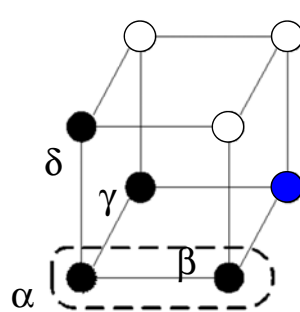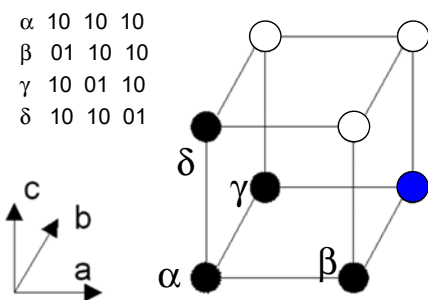α 10 10 10
β 01 10 10
γ 10 01 10
δ 10 10 01



01 10 10 → 11 10 10 **OK**
11 10 10 → 11 11 10 **OK**
11 11 10 → 11 11 11 **X**



F updated to :

11	11	10
10	10	01

10 10 01 → 11 10 01 **X**
10 10 01 → 10 11 01 **X**
10 10 01 → 10 10 11 **OK**

Expanded cover :

11	11	10
10	10	11

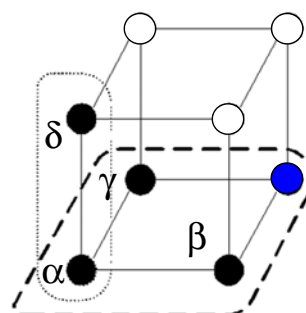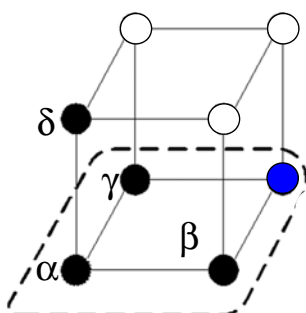

Reduce (1/2)

- Decrease the size of each implicant of a given cover F
 - successive expansion may lead to smaller cover
 - A reduced implicant is valid when, along with the remaining implicants, it still covers the function
 - The reduced cover has the same cardinality as the original one
- Let $\alpha \in F$ be an implicant and $Q = F \cup F^{DC} - \{\alpha\}$
 - The maximally reduced cube is

$$\alpha'' = \alpha \cap \text{supercube}(Q_{\alpha}') \quad // \text{ the part not covered by other implicants}$$
- $\alpha \# Q = \alpha \cap Q'$ can yield a set of cubes

$$\begin{aligned} \alpha'' &= \alpha \cap \text{supercube}(Q') \\ &= \alpha \cap \text{supercube}((\alpha \cap Q_{\alpha}') \cup (\alpha' \cap Q_{\alpha}')) \\ &= \alpha \cap \text{supercube}(Q_{\alpha}') \end{aligned}$$



Reduce (2/2)

- Sorting the implicants
 - Weight the implicants as for the Expand operator
 - Sort implicants in **descending** order of weight
 - First process those that overlap many other implicants
 - Lower as many * as possible to 1 or 0
- Replacing each implicant by the maximally reduced one

$F: \alpha \quad 11 \quad 11 \quad 10$

$\beta \quad 10 \quad 10 \quad 11$

column count vector = $[212121]^T$

weight vector = $[8,7]$

Reduce α first → fail

Reduce β :

$$\begin{aligned} Q &= F \cup F^{DC} - \{\beta\} = \{\alpha, \beta\} - \{\beta\} \\ &= 11 \quad 11 \quad 10 \quad // \text{ only } \alpha \text{ is left} \end{aligned}$$

$$Q' = 11 \quad 11 \quad 01, \quad Q_{\beta}' = Q'$$

$$\text{supercube}(Q_{\beta}') = Q' \quad // \text{ not in } Q$$

$$\beta'' = \beta \cap Q' = 10 \quad 10 \quad 01$$

Reduced cover is

11 11 10

10 10 **01**

$\beta'' \rightarrow$ In β but not in Q



Outline

- Synthesis overview
- RTL synthesis
- Two-level logic optimization
- Multi-level logic optimization
- Technology mapping
- Timing analysis
- Timing optimization
- Synthesis for low power



Multi-Level Logic Optimization

- Level: maximum number of gates cascaded in series between the inputs and outputs of a network
 - Can be considered as an indication for worst-case delay
 - Assume all variables and their complements are available
- Two-level networks have the least depth, not least area
 - It's possible to further reduce the number of gates by increasing the logic levels and reusing existing logic gates
 - Common factors or kernel extraction
 - Common expression resubstitution

- Example:

$$\begin{aligned} f1 &= abcd + abce + \bar{a}\bar{b}cd + \bar{a}\bar{b}cd + \bar{a}c + cdf + \bar{a}\bar{b}cde + \bar{a}\bar{b}cdf \\ f2 &= bdg + \bar{b}dfg + \bar{b}dg + \bar{b}deg \end{aligned}$$




$$\begin{aligned} f1 &= c(\bar{a} + x) + \bar{a}\bar{c}\bar{x} \\ f2 &= gx \\ x &= d(b + f) + \bar{d}(\bar{b} + e) \end{aligned}$$



Multi-Level Logic

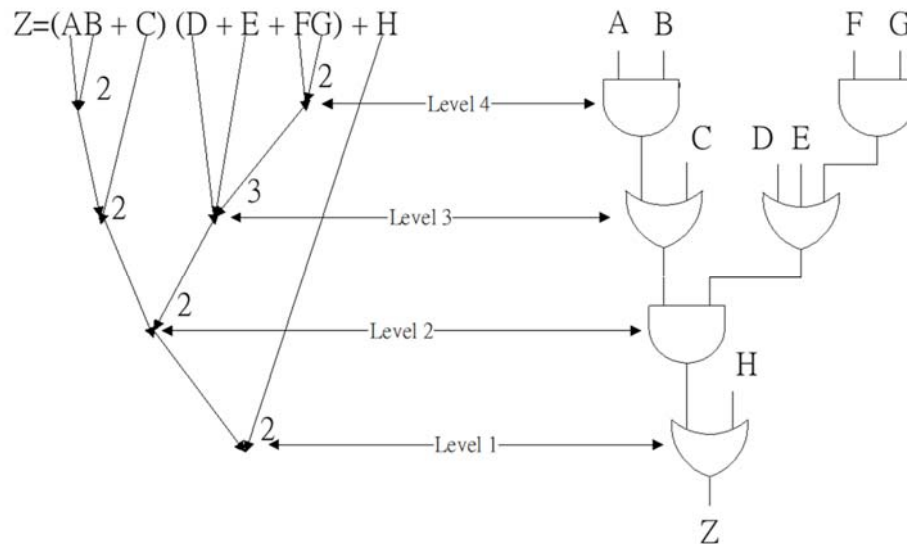- Multi-level logic:
 - A set of logic equations with no cyclic dependencies
- Example: $Z = (AB + C)(D + E + FG) + H$
 - 4-level, 6 gates, 13 gate inputs




Multi-Level v.s. Two-Level

- | | |
|--|--|
| <ul style="list-style-type: none"> • Two-level: <ul style="list-style-type: none"> – Often used in control logic design – $f_1 = x_1x_2 + x_1x_3 + x_1x_4$ – $f_2 = x_1'x_2 + x_1'x_3 + x_1x_4$ – Only x_1x_4 shared – Sharing restricted to common cube | <ul style="list-style-type: none"> • Multi-level: <ul style="list-style-type: none"> – Datapath or control logic design – Can share $x_2 + x_3$ between the two expressions – Can use complex gates – $g_1 = x_2 + x_3$ – $g_2 = x_1x_4$ – $f_1 = x_1y_1 + y_2$ – $f_2 = x_1'y_1 + y_2$ – (y_i is the output of gate g_i) |
|--|--|

Factored Forms (1/2)

- A *factored form* is defined recursively by the following rules:
 - A literal is a factored form
 - A sum of two factored form is a factored form
 - A product of two factored forms is a factor form
- A factored form describes an implementation of the function as a complex gate
 - Any depth of sum-of-product
- Ex: a
a'
ab'c
ab + c'd
(a + b)(c + a' + de) + f

Factored Forms (2/2)

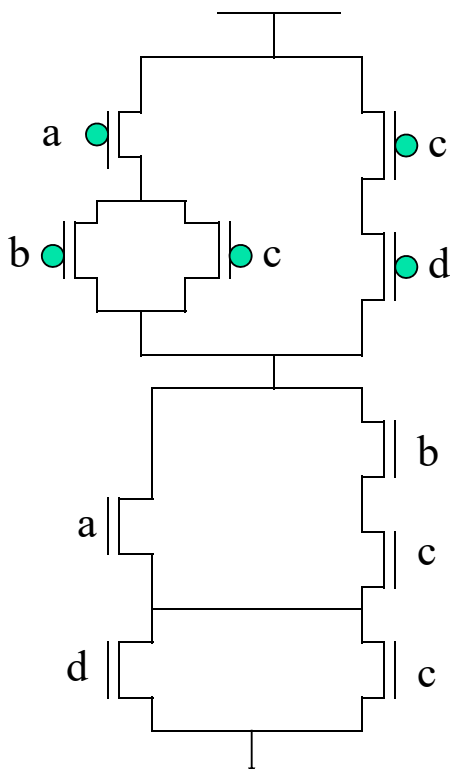


- A CMOS complex gate implementing $f = ((a + bc)(c + d))'$
 $2 \times \text{literal count} = \# \text{ transistors}$
- Adv:
 - Nature multi-level representation
 - Good estimate of the complexity of function
 - Represent both the function and its complement
- Disadv:
 - More difficult to manipulate than two-level form
 - Lack of the notion of optimality


Boolean Network

- Directed acyclic graph (DAG)
- Each source node is a primary input
- Each sink node is a primary output
- Each internal node represents an equation
- Arcs represent variable dependencies

fanin of y : a, b
fanout of x : F

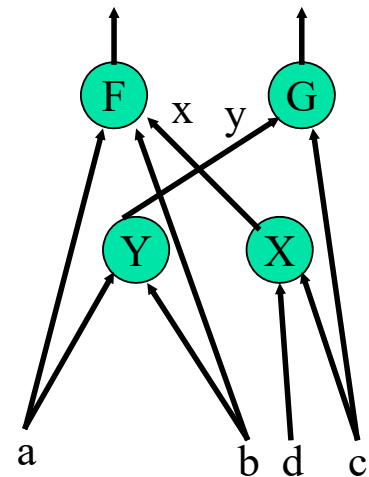

Boolean Network : An Example

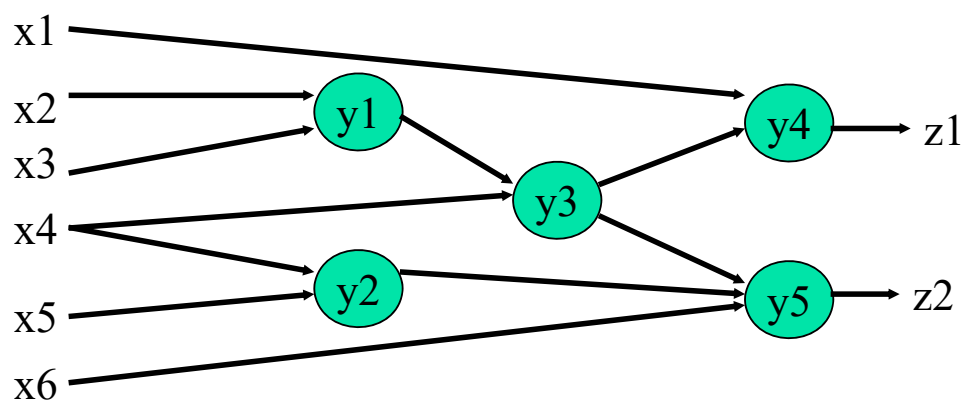

$$y1 = f_1(x2, x3) = x2' + x3'$$

$$y2 = f_2(x4, x5) = x4' + x5'$$

$$y3 = f_3(x4, y1) = x4'y1'$$

$$y4 = f_4(x1, y3) = x1 + y3'$$

$$y5 = f_5(x6, y2, y3) = x6y2 + x6'y3'$$



Multi-Level Logic Optimization

- Technology independent
- Decomposition/Restructuring
 - Algebraic
 - Functional
- Node optimization
 - Two-level logic optimization techniques are used



Decomposition / Restructuring

- Goal : given initial network, find best network
- Two problems:
 - Find good **common subfunctions**
 - How to perform **division**
- Example:

$$f_1 = abcd + abce + ab'cd' + ab'c'd' + a'c + cdf + abc'd'e' + ab'c'df'$$

$$f_2 = bdg + b'dfg + b'd'g + bd'eg$$

minimize (in sum-of-products form):

$$f_1 = bcd + bce + b'd' + b'f + a'c + abc'd'e' + ab'c'df'$$

$$f_2 = bdg + dfg + b'd'g + d'eg$$

decompose:

$$f_1 = c(a' + x) + ac'x' \quad x = d(b + d) + d'(b' + e)$$

$$f_2 = gx$$




Basic Operations (1/2)

1. decomposition

(single function)

$$f = abc + abd + a'c'd' + b'c'd'$$

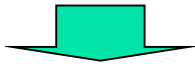

$$f = xy + x'y'$$

$$x = ab$$

$$y = c + d$$


2. extraction

(multiple functions)

$$f = (az + bz')cd + e$$

$$g = (az + bz')e'$$

$$h = cde$$

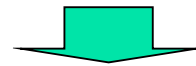

$$f = xy + e$$

$$g = xe'$$

$$h = ye$$

$$x = az + bz'$$

$$y = cd$$

Basic Operations (2/2)

3. factoring

(series-parallel decomposition)

$$f = ac + ad + bc + bd + e$$



$$f = (a + b)(c + d) + e$$

4. substitution

(with complement)

$$g = a + b$$

$$f = a + bc + b'c'$$



$$f = g(a + c) + g'c'$$

5. elimination

$$f = ga + g'b$$

$$g = c + d$$



$$f = ac + ad + bc'd'$$

$$g = c + d$$

**“Division” plays
a key role !!**

Division

- Division: p is a Boolean divisor of f if $q \neq \phi$ and r exist such that $f = pq + r$
 - p is said to be a factor of f if in addition $r = \phi$:
$$f = pq$$
 - q is called the **quotient**
 - r is called the **remainder**
 - q and r are **not unique**
- **Weak division**: the unique algebraic division such that r has as few cubes as possible
 - The quotient q resulting from weak division is denoted by f / p (it is **unique**)



Weak Division Algorithm (1/2)

Weak_div(f, p):

U = Set $\{u_j\}$ of cubes in f with literals not in p deleted

V = Set $\{v_j\}$ of cubes in f with literals in p deleted

/* note that $u_j.v_j$ is the j -th cube of f */

$V^i = \{v_j \in V : u_j = p_j\}$

$q = \cap V^i$

$r = f - pq$

return(q, r)



Weak Division Algorithm (2/2)

- Example

common expressions

$$f = acg + adg + ae + bc + bd + be + a'b$$

$$p = ag + b$$

$$U = ag + ag + a + b + b + b + b$$

$$V = c + d + e + c + d + e + a'$$


$$V^{ag} = c + d$$

$$V^b = c + d + e + a'$$

$$q = c + d = f/p$$

Algebraic Substitution (1/3)

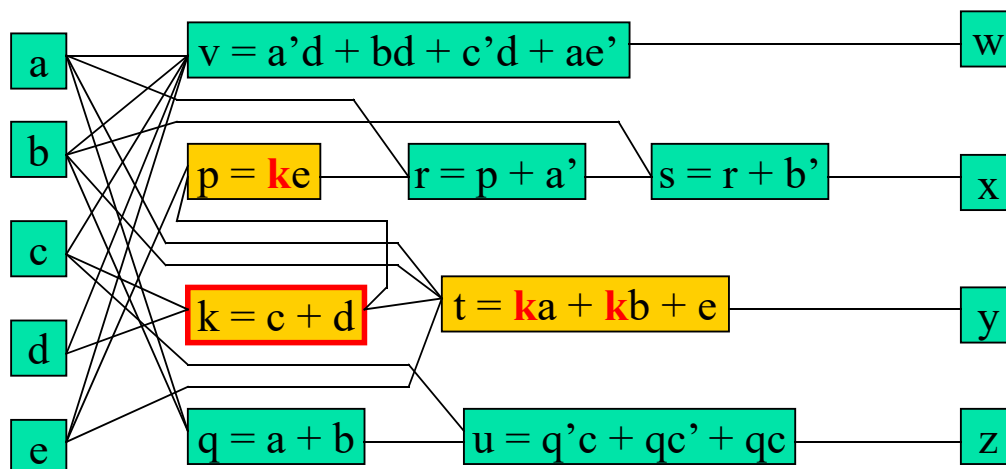
- Idea: An existing node in a network may be a useful divisor in another node.



$$f_t = ka + kb + e$$

$$f_q = a + b$$

Algebraic Substitution (2/3)

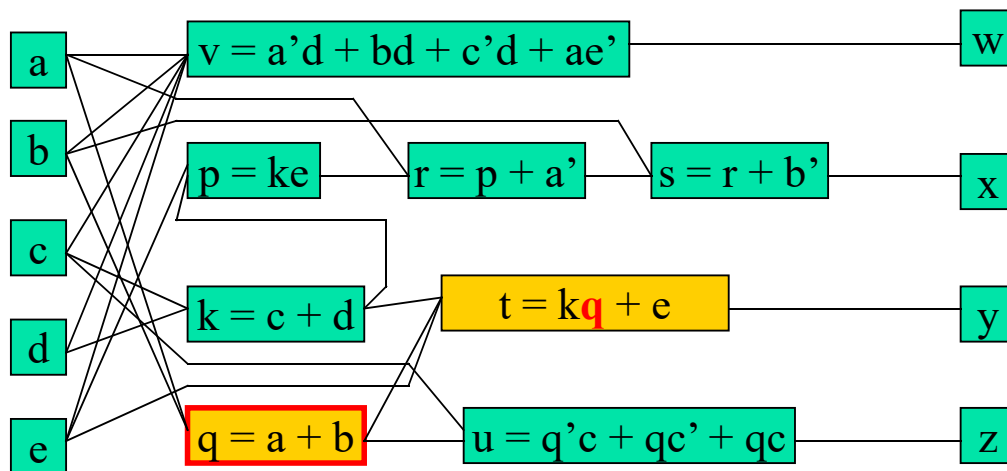

$$f_t = kq + e$$

Algebraic Substitution (3/3)

- Consist of the process of dividing the function f_i at node i in the network by the function f_j (or by f_j') pairwise
- During substitution, f_i is transformed into

$$f_i = (f_i/f_j)y_j + (f_i/f_j')y_j' + r$$
 if f_i/f_j and/or f_i/f_j' are not null
- No need to try all pairs. The cases where f_j is not an algebraic divisor of f_i can be excluded
 - f_j contains a literal not in f_i
 - f_j contains more terms than f_i
 - for any literal, the count in f_j exceeds that in f_i
 - f_i is f_j 's transitive fanin (cycle)

Algebraic Divisor

- Example:

$$X = (a + b + c)de + f$$

$$Y = (b + c + d)g + aef$$

$$Z = aeg + bc$$

- Single-cube divisor: ae
- Multiple-cube divisor: $b + c$
- Extraction of **common sub-expression** is a global area optimization effort



Kernels and Kernel Intersections

- An expression is **cube-free** if no cube divides the expression evenly
 - e.g., $ab + c$ is cube-free; $ab + ac$ and abc are not cube-free
 - A cube-free expression must have more than one cube
- The **primary divisors** of an expression f are the set of expressions

$$D(f) = \{f/c \mid c \text{ is a cube}\}$$

- The **kernels** of an expression f are the set of expressions
$$K(f) = \{g \mid g \in D(f) \text{ and } g \text{ is cube free}\}$$



Co-Kernels

- A cube c used to obtain the kernel $k = f/c$ is called a **co-kernel** of k
 - $C(f)$ is used to denote the set of co-kernels of f
- Example

$$\begin{aligned} x &= adf + aef + bdf + bef + cdf + cef + g \\ &= (a + b + c)(d + e)f + g \end{aligned}$$


Kernel	Co-kernel
$a + b + c$	df, ef
$d + e$	af, bf, cf
$(a + b + c)(d + e)f + g$	1

- Kernels and co-kernels can help to find common divisors between expressions



Kerneling Illustrated
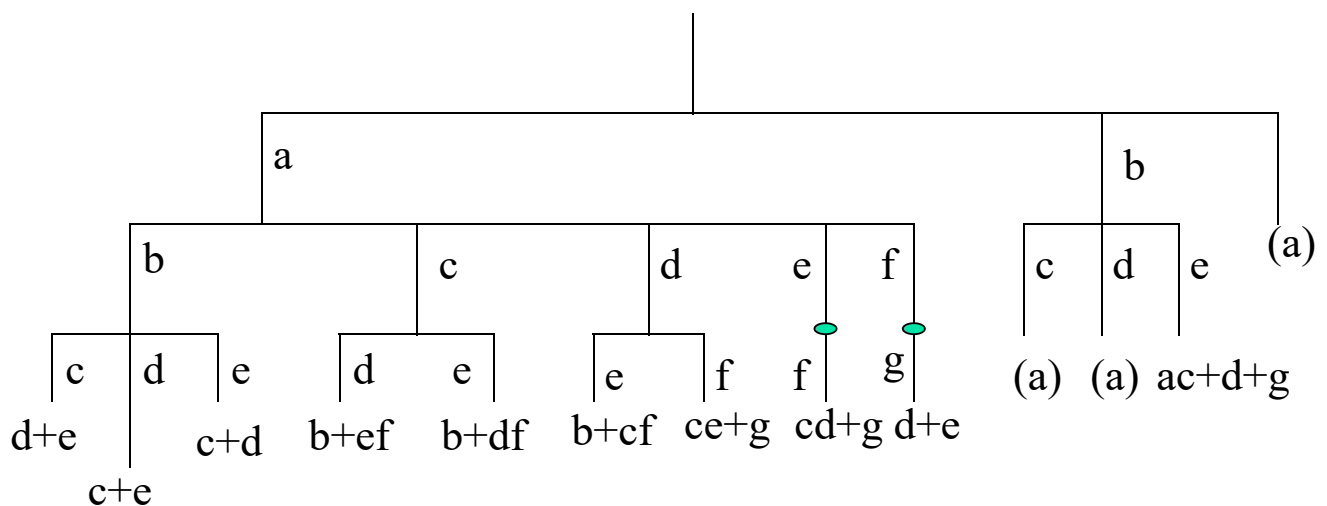
$$abcd + abce + adfg + aefg + adbe + acdef + beg$$



Cube-Literal Matrix & Rectangles (1/2)

- Cube-literal matrix
 - Each matrix element indicates if this literal appears in the cube
- Ex: $f = x_1x_2x_3x_4x_7 + x_1x_2x_3x_4x_8 + x_1x_2x_3x_5 + x_1x_2x_3x_6 + x_1x_2x_9$

	x_1	x_2	x_3	x_4	x_5	x_6	x_7	x_8	x_9
$x_1x_2x_3x_4x_7$	1	1	1	1	0	0	1	0	0
$x_1x_2x_3x_4x_8$	1	1	1	1	0	0	0	1	0
$x_1x_2x_3x_5$	1	1	1	0	1	0	0	0	0
$x_1x_2x_3x_6$	1	1	1	0	0	1	0	0	0
$x_1x_2x_9$	1	1	0	0	0	0	0	0	1



Cube-Literal Matrix & Rectangles (2/2)

- A **rectangle** (R, C) of a matrix A is a subset of rows R and columns C such that

$$A_{ij} = 1 \forall i \in R, j \in C$$

- Rows and columns need not be continuous
- A **prime rectangle** is a rectangle not contained in any other rectangle
 - A prime rectangle indicates a co-kernel kernel pair

- Example:

$$R = \{\{1, 2, 3, 4\}, \{1, 2, 3\}\}$$

- co-kernel: $x_1x_2x_3$
- kernel: $x_4x_7 + x_4x_8 + x_5 + x_6$

	x_1	x_2	x_3	x_4
$x_1x_2x_3x_4x_7$	1	1	1	1
$x_1x_2x_3x_4x_8$	1	1	1	1
$x_1x_2x_3x_5$	1	1	1	0
$x_1x_2x_3x_6$	1	1	1	0
$x_1x_2x_9$	1	1	0	0



Rectangles and Logic Synthesis

- Kernels \Leftrightarrow prime rectangles of the cube-literal matrix
- Optimum selection of kernels \Leftrightarrow **rectangle covering**
 - Kernel intersection \Leftrightarrow finding rectangles

- Ex: single cube extraction

$$F = abc + abd + eg$$

$$G = abfg$$

$$H = bd + ef$$

$$(\{1,2,4\}, \{1,2\}) \Leftrightarrow ab$$

$$(\{2,5\}, \{2,4\}) \Leftrightarrow bd$$

$$F = Xc + XY + eg, \quad X = ab$$

$$G = Xfg, \quad Y = bd$$


$$H = Y + ef$$

		<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
		1	2	3	4	5	6	7
<i>abc</i>	1	1	1	1	0	0	0	0
<i>abd</i>	2	1	1	0	1	0	0	0
<i>eg</i>	3	0	0	0	0	1	0	1
<i>abfg</i>	4	1	1	0	0	0	1	1
<i>bd</i>	5	0	1	0	1	0	0	0
<i>ef</i>	6	0	0	0	0	1	1	0




Kernel Extraction (1/2)

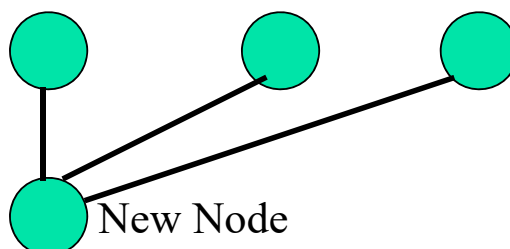- 1. Find all kernels of all functions
- 2. Choose one with best "value"
- 3. Create new node with this as function
- 4. Algebraically substitute new node everywhere
- Repeat 1,2,3,4 until best value \leq threshold




Kernel Extraction (2/2)

- After

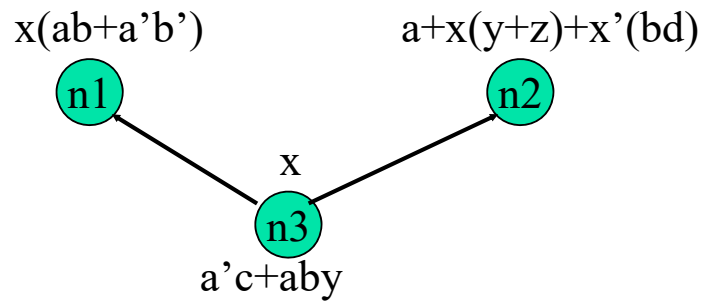

- Before

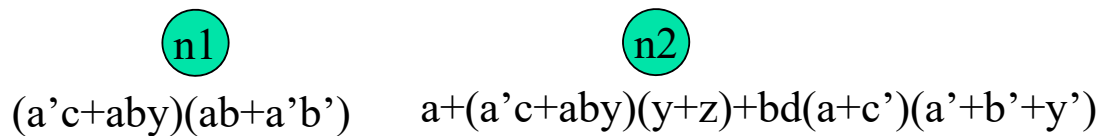

Literals after = 5+7+5=17 Literals before = 9+15 = 24
 before – after = value = 7

Example – Decomposition (1/2)

Original: $f_1 = ab(c(d + e) + f + g) + h$ (literal = 8+8 = 16)
 $f_2 = ai(c(d + e) + f + j) + k$

Kernel extraction: (literal = 2+7+7 = 16)

$$K^0(f_1) = K^0(f_2) = \{d + e\}$$

$$l = d + e$$



$$f_1 = ab(cl + f + g) + h$$

$$f_2 = ai(cl + f + j) + k$$

Kernel extraction: (literal = 2+3+5+5 = 15)

$$K^0(f_1) = \{cl + f + g\}$$

$$K^0(f_2) = \{cl + f + j\}$$

$$K^0(f_1) \cap K^0(f_2) = cl + f$$



$$m = cl + f$$

$$f_1 = ab(m + g) + h$$

$$f_2 = ai(m + j) + k$$

Cube extraction: (literal = 2+3+2+5+5 = 17)


$$n = am$$



$$f_1 = b(n + ag) + h$$

$$f_2 = i(n + aj) + k$$

Example – Decomposition (2/2)

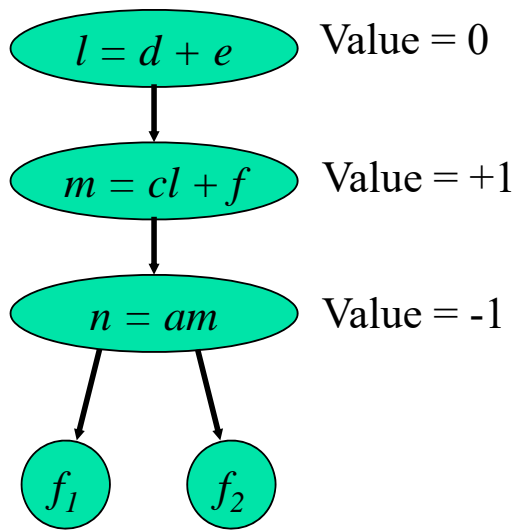

- Eliminate -1

$$n = a(c(d + e) + f)$$

$$f_1 = b(n + ag) + h$$

$$f_2 = i(n + aj) + k$$

merge 3 levels
together

